

Digital System Design - Assignment 4

Name: Megh Manoj Bhalerao

Roll No: 16EE234

1) a) 8×8 array multiplier:

For $n \times n$ array multiplier:

n^2 AND gate, $n(n-2)$ Full adders, $n-1$ half adders.

\therefore 64 AND gates

48 Full adders

8 Half adders

b) 8×8 array multiplier

t_g (AND gate delay) = $1ns$

t_{ad} (HA / FA delay) = $2ns$

We know that, the longest path from input to output goes through $n-1$ adders in the top row, $n-1$ adders in the bottom row and $n-3$ adders in the middle row.

Hence, worst case multiply time is:

$$(3n-4)t_{ad} + t_g = (3 \times 8 - 4)2ns + 1ns$$

$$= \underline{\underline{41ns}}$$

Worst case can be improved to $2nt_{ad} + t_g$ by forwarding carry from each adder to diagonally lower adder.

⊗ Hence, the time becomes...

$$2 \times 8 \times 2 \text{ ns} + 1 \text{ ns} = \underline{\underline{33 \text{ ns}}}$$

c) Assuming worst case time (time taken by array multiplier is 41 ns).

In an add and shift multiplier : the worst case number of changes in state is $2n+2$, which takes $2n+1$ clock cycles, assuming 'n' is the # of bits multiplier.

∴ For 8 bit add-shift multiplier :-

$$\therefore 2 \times 8 + 1 = 17 \text{ clock cycles}$$

$$17 \text{ clock cycles} \rightarrow 41 \text{ ns}$$

$$1 \text{ clock} \rightarrow \frac{41 \text{ ns}}{17}$$

$$T = (\text{time period of 1 clock cycle}) : \frac{41}{17} \text{ ns} = 2.41 \text{ ns}$$

$$f(\text{of clock cycle}) = 0.4147 \times 10^9 \text{ Hz (f of clock)}$$

2) a) 16×16 array multiplier

AND gates = $n^2 = 256$ AND gates


$$\# \text{ of Adders (HA \& FA)} = \underbrace{n(n-2)}_{\text{FA}} + \underbrace{n}_{\text{HA}} = 16 \times 14 + 16 = \underline{\underline{240 \text{ adders}}}$$

b) Worst case/Longest delay in standard array multiplier representation :

$(3n-4)t_{ad} + t_g \rightarrow$ Without improvement

$2nt_{ad} + t_g \rightarrow$ With improvement \rightarrow forward carry from each adder to diagonally lower adder

3) a) Ripple carry adder

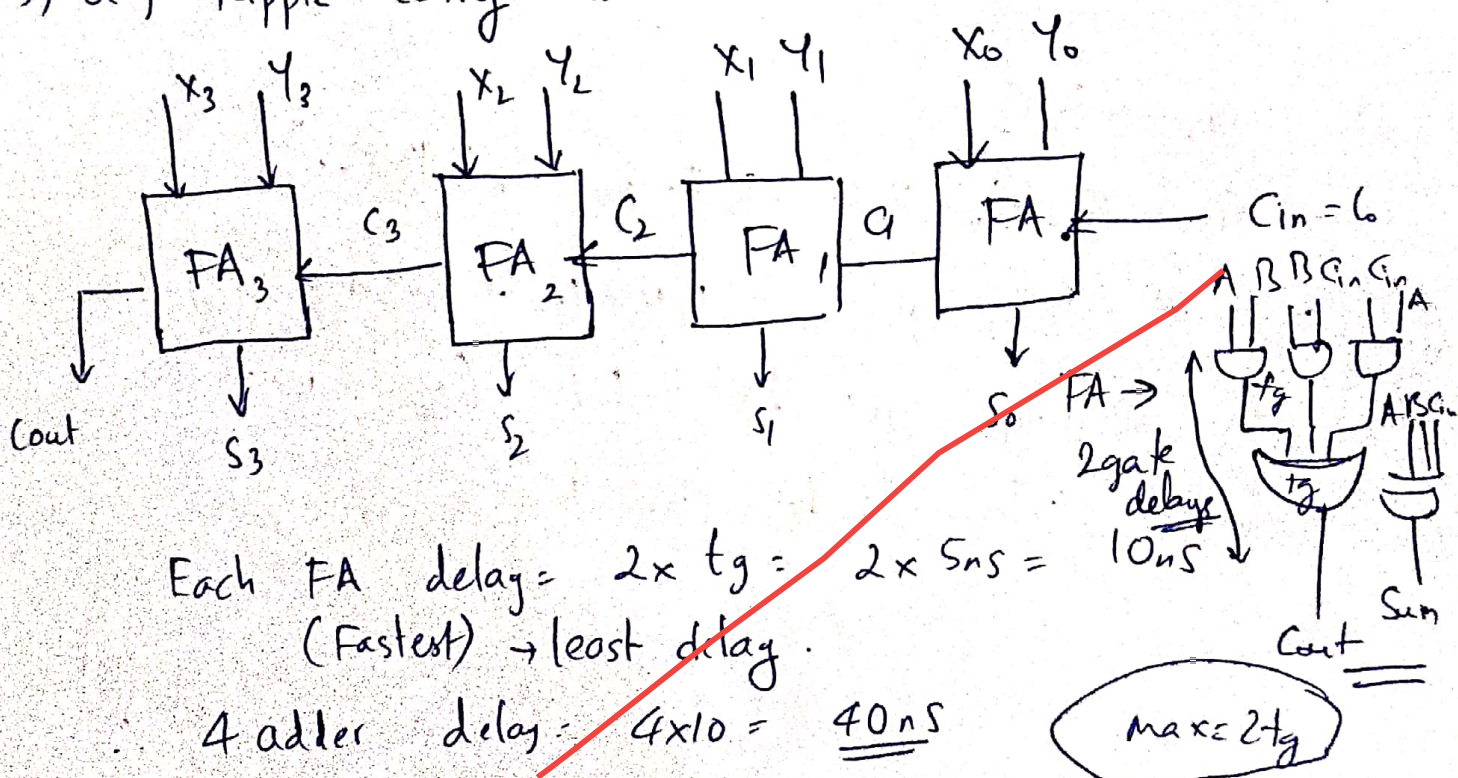

3) b) The Carry look-ahead adder is the fastest bit adder.
The CLA predicts the carry before it is calculated.

$$C_i = G_i + P_i \cdot C_{i-1}$$

$$G_i = A_i \cdot B_i, \quad P_i = A_i \oplus B_i$$

⊗ From this recursive equation, all the carries can be predicted in advance.
2nd last ~~last~~ carry in a 4-bit adder.

$$C_2 = G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_{-1})$$

$$\textcircled{C_2} = G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_{-1}) =$$

$$G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{-1}$$

↓
Directly ~~last~~ ^{second-last} bit

$$C_3 = G_3 + P_3 C_2$$

$$= G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{-1})$$

$$\textcircled{C_3} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 \textcircled{C_{-1}}$$

↳ Can directly get last bit. (No need to calculate intermediate circuit.)

The general form for the delay of CLA with L -levels is $2(2L-1)+4 = 4L+2$ gate delays

Hence # of levels for 4 bit CLA (fast) = 1


$\therefore 4 \times 1 + 2$ gate delay

$\Rightarrow 6 t_g = 6 \times 5ns = \textcircled{30ns}$ delay in CLA

4) 1001 detector:-

of sq. boxes in ASM = # of states of the system.


State diagram for 1001 detector

 

1001 - detector
1000


$S_0 \rightarrow$ Reset state

State diagram:

 


→ Moore state diagram has 5 - states
 → Hence ASM representation will have 5 state boxes.

5) Moore Machine Representation:

 

Mealy Machine Representation:

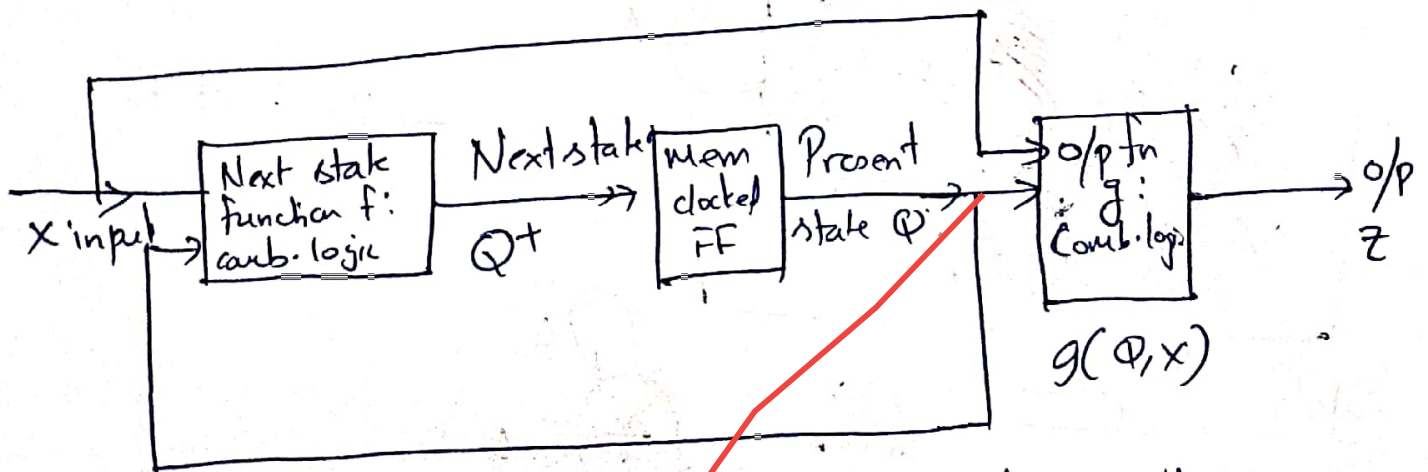

② Hence, it can be seen here that by setting the $g(Q, X)$ function in the mealy machine such that 'X' has no effect on the output, the mealy representation becomes a moore representation i.e. $g(Q)$

⑤ However, the converse $g(Q) \rightarrow g(Q, X)$ is not possible since we need to add another dependency on X , but there is no such provision made in the machine representation for a Moore machine.

Hence:

- ① Mealy can be represented as Moore.
- ② But Moore can't be represented as Mealy.

6) The ASM can be converted into the state table for easier analysis.

(2 states)

$X = \text{don't care}$

→ State table from the ASM diagram:

Present state	Next state (AB form)		Output (Z)		
	00	01	10	11	
s_0	s_0	s_0	s_1	s_1	0
s_1	s_1	s_0	s_1	s_0	1

→ Encoding the states as numbers:

PS (Q)	NS (I/p = AB form)				Output Z
	00	01	10	11	
0	0	0	1	1	0
1	1	0	1	0	1

→ Truth table for the corresponding state table

Q	A	B	Q^+	Z
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	0	1
1	1	0	1	1
1	1	1	0	1

$$Z = Q$$

From TT

$$Q^+ = \bar{Q}A + Q\bar{B}$$

This is the characteristic eqn (excitation eq) of A JK Flip flop where

$$\begin{aligned} J &= A \\ K &= B \end{aligned}$$

7) To determine the MAX number of transition arrows leaving and entering the state.

⊗ 3 FF


⊗ 2 INPUTS \rightarrow AB } Moore machine

⊗ 5 outputs \rightarrow

\hookrightarrow Doesn't matter since state dependent

3 FF $\rightarrow 2^3 = 8$ states max.

I/P = AB

 

Max # of arrows leaving a state = 4 ($2^2 \rightarrow 2 \text{ I/P}$)

Max # of arrows entering a state \Rightarrow If all states point to one of the state (say S_1) \Rightarrow

of incoming arrows on S_1 are :


$(2^3 - 1) \times 2^2 = 28$ inbound arrow at most for any given state

8) N states \rightarrow # of flip-flops are

$$\lceil \log_2(N) \rceil + 1 = NF$$

$\lceil \cdot \rceil$ denotes the step-function or Greatest Integer function

9) BCD Adder circuit diagram:

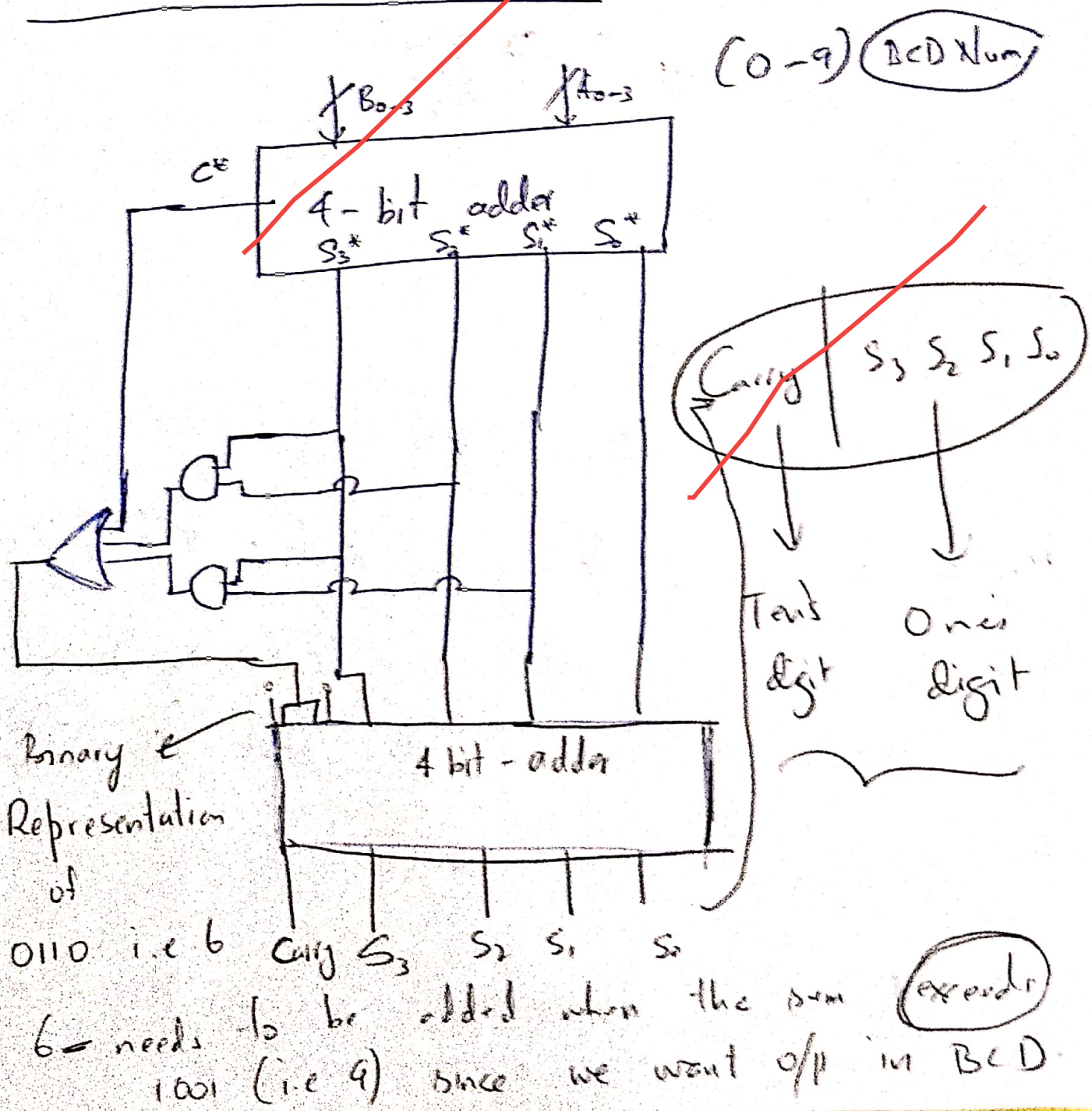

Hence, the statement is FALSE.

Since if result is $\Rightarrow 1001$, 0110 must be added


Greater than (Not less-than)

10) 4-bit adder:

14 \rightarrow in binary form - 1110 $\rightarrow A$

7 \rightarrow in binary 4bit-form - 0111 $\rightarrow B$

 \therefore The 4 bit adder will look like:



$$C_3 C_2 C_1 = 110$$

$$C_4 S_3 S_2 S_1 S_0 : 10101 \rightarrow \textcircled{21} \text{ (Correct Sum)}$$