

# Synthesis of clocked sequential circuits

# Synthesis of clocked sequential circuit

- **Clocked sequential circuit** – a logic design circuit which includes flip-flops with clock inputs.
- May or may not include combinational logic gates.
- **State table and state diagram** – describe the behavior of a sequential circuit.

# Synthesis of clocked sequential circuit


- Behavior of a clocked sequential circuit - determined from the inputs, outputs and the state of its flip-flops.
- Outputs and next state are both – function of the inputs and the present state.
- Analysis of a sequential circuit – obtaining a table or a diagram for the time sequence of inputs, outputs and internal states.

# Synthesis of clocked sequential circuit

- **State equations:** algebraic description of behavior of a clocked sequential circuit.

Transition equation – specifies the next state as a function of the present state and inputs.
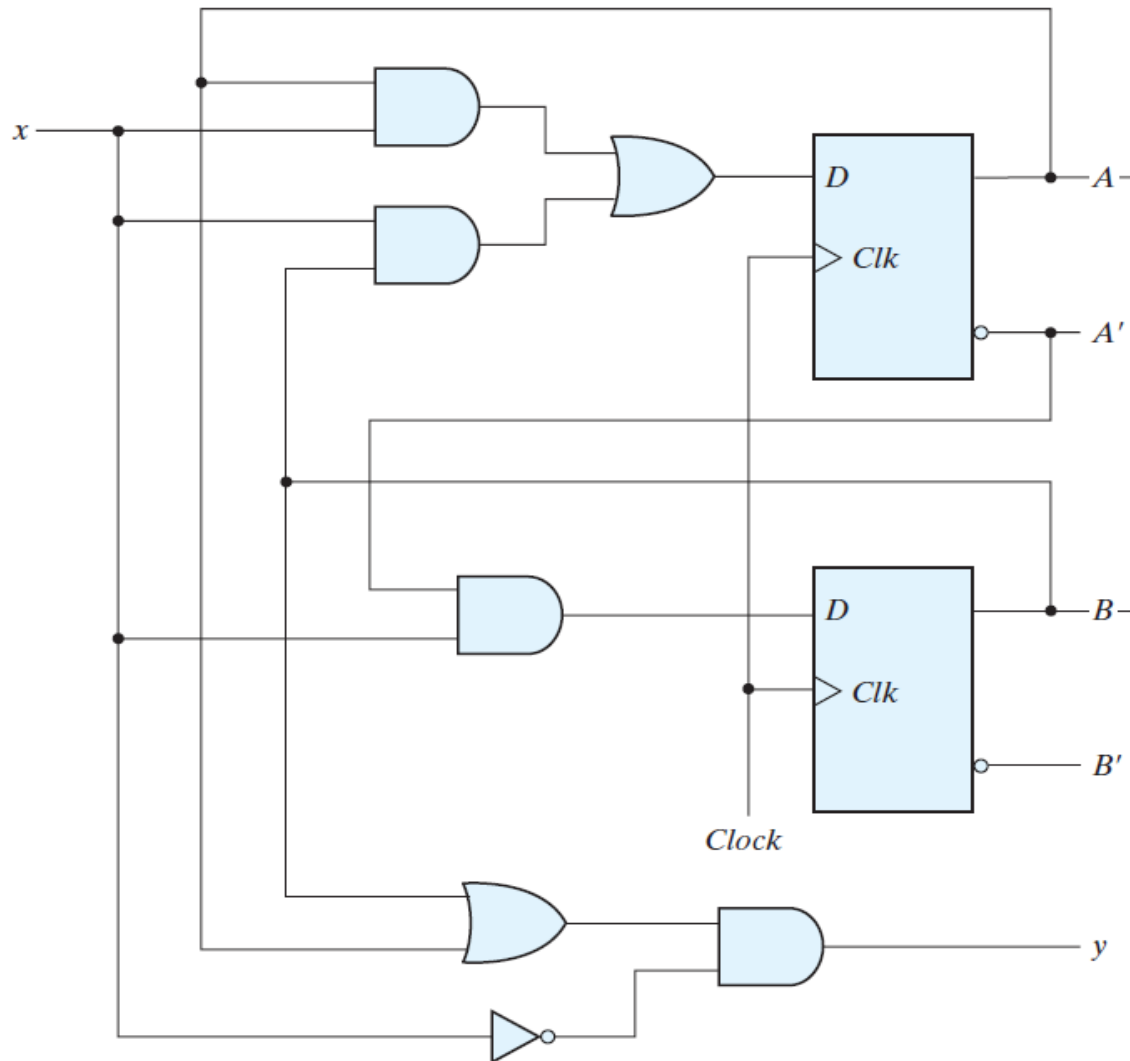
# Synthesis of clocked sequential circuit



$$A(t + 1) = Ax + Bx$$

$$B(t + 1) = A'x$$

$$y = (A + B)x'$$

# Synthesis of clocked sequential circuit

$$A(t + 1) = Ax + Bx$$

$$B(t + 1) = A'x$$

$$y = (A + B)x'$$

$$A(t + 1) = A(t)x(t) + B(t)x(t)$$

$$B(t + 1) = A'(t)x(t)$$

$$y(t) = [A(t) + B(t)]x'(t)$$

# Synthesis of clocked sequential circuit

- sequential circuit with  $m$  flip-flops and  $n$  inputs needs -  $2^{m+n}$  rows in the state table.
- Binary numbers from 0 through  $2^{m+n} - 1$  are listed under the present-state and input columns.
- Next-state section has  $m$  columns, one for each flip-flop.
- Output section - No.of columns = No. of output variables.

# State table - 1

Present State		Input	Next State		Output
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0




# State table - 2

## Second Form of the State Table

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>y</i>	<i>y</i>
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0


# State diagram

 

A directed line connecting a circle with itself - no change of state occurs.

- State diagrams - Graphical representation of information available in state-table.
- Each state – represented by a circle.
- Transition between the states – directed lines connecting the states.
- Input during the present state / output during the present state for the given input.

# sequential circuit – example 2

 


Sequential circuit with  $D$  flip-flop

# Synthesis of clocked sequential circuit

Present state	Inputs		Next state
$A$	$x$	$y$	$A$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


(b) State table

 

(c) State diagram

Sequential circuit with *D* flip-flop

# Sequential circuit – example 3

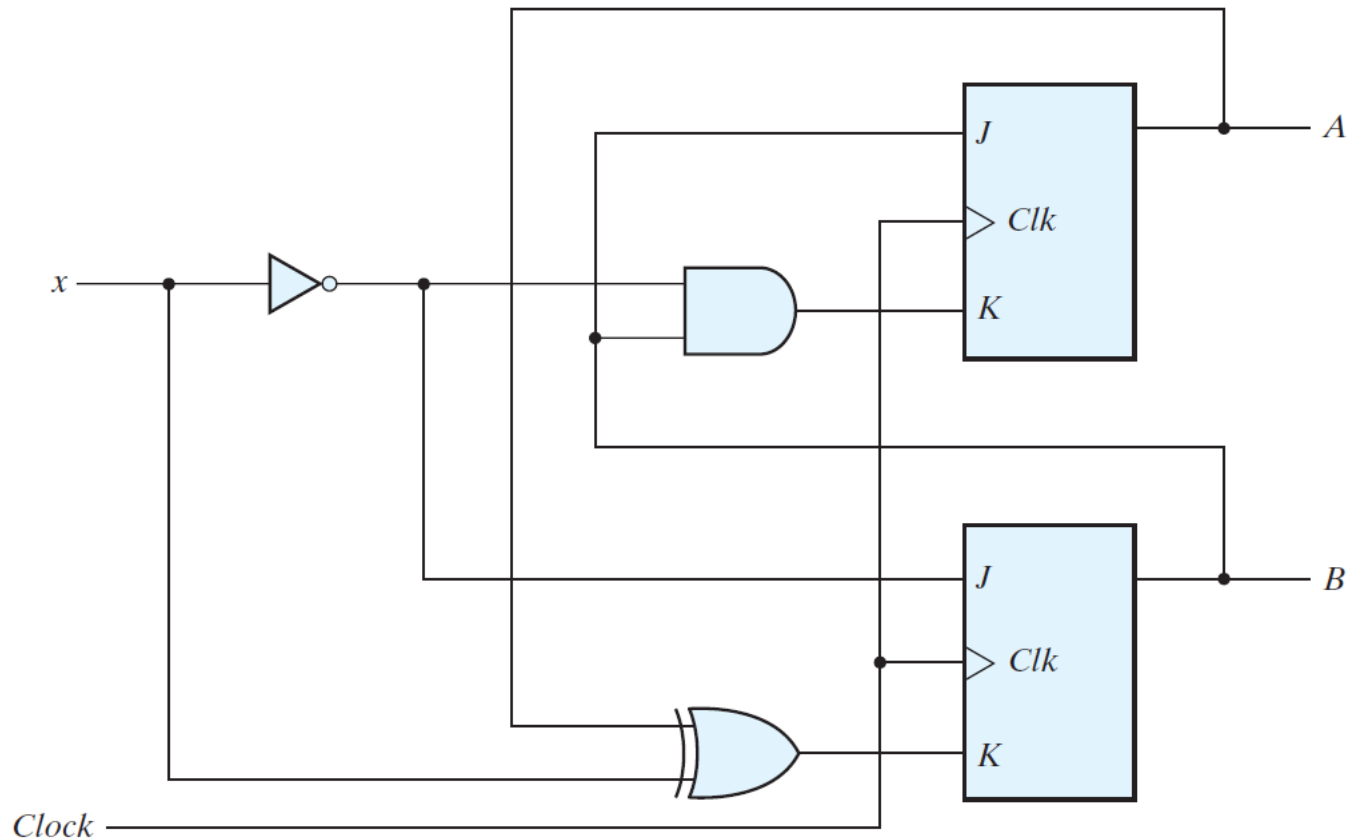

Sequential circuit with  $J/K$  flip-flop


# Synthesis of clocked sequential circuit

*State Table for Sequential Circuit with JK Flip-Flops*

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0


Sequential circuit with JK flip-flop
 
# Synthesis of clocked sequential circuit




State diagram

# Sequential circuit – example 4

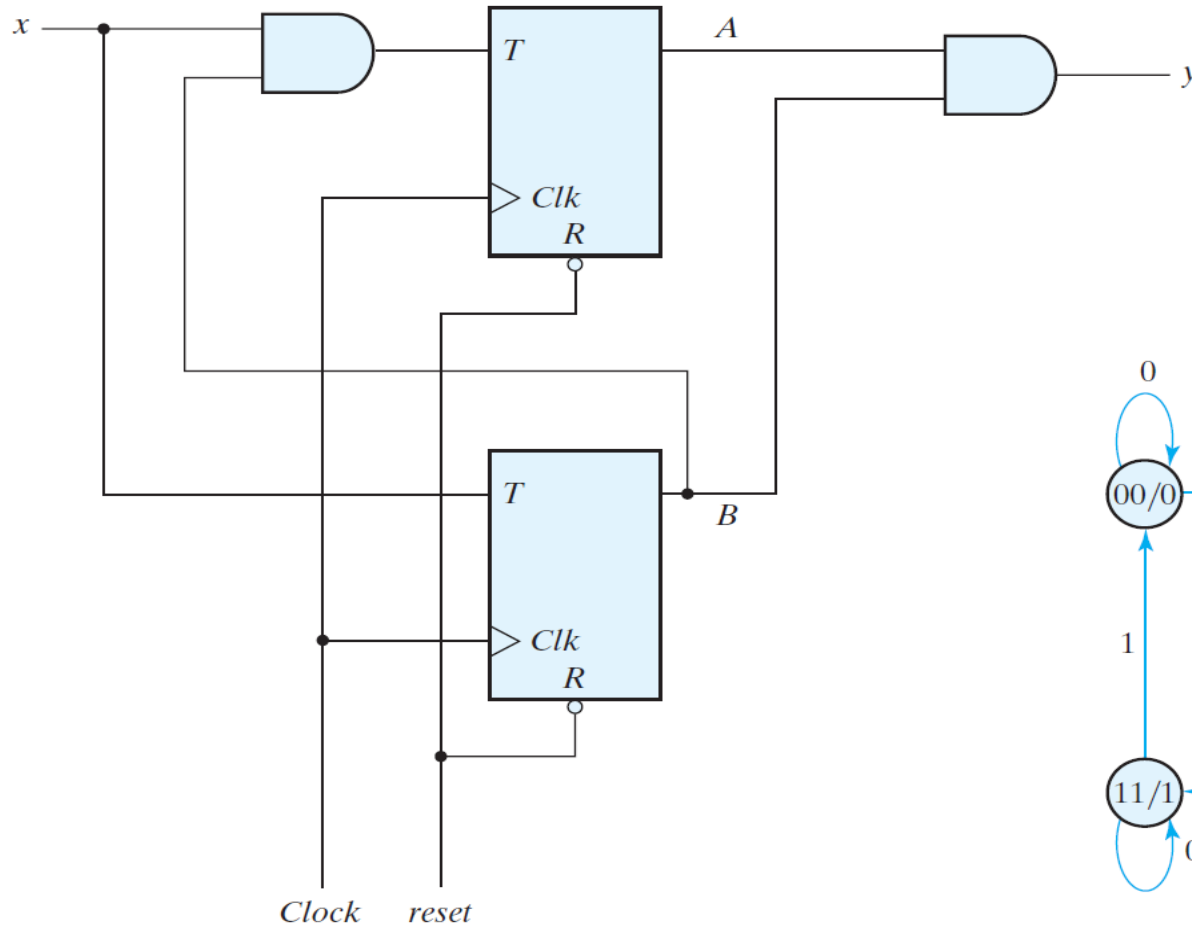

(a) Circuit diagram

 

(b) State diagram

Sequential circuit with  $T$  flip-flops

DR PADMAVATHI L, NITK





# Synthesis of clocked sequential circuit

*State Table for Sequential Circuit with T Flip-Flops*


<b>Present State</b>		<b>Input</b>	<b>Next State</b>		<b>Output</b>
<b>A</b>	<b>B</b>		<b>A</b>	<b>B</b>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

# Mealy and Moore state machines

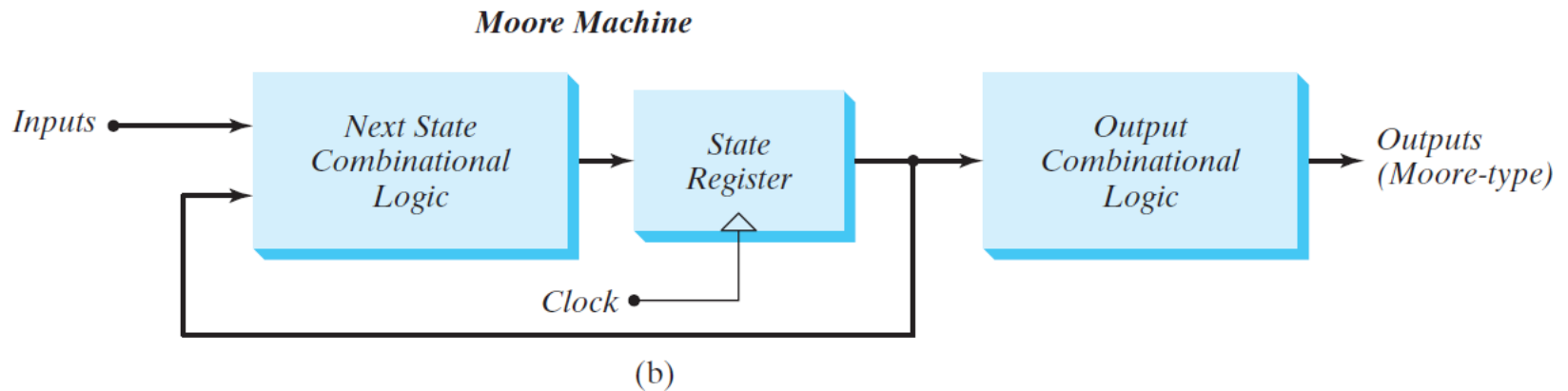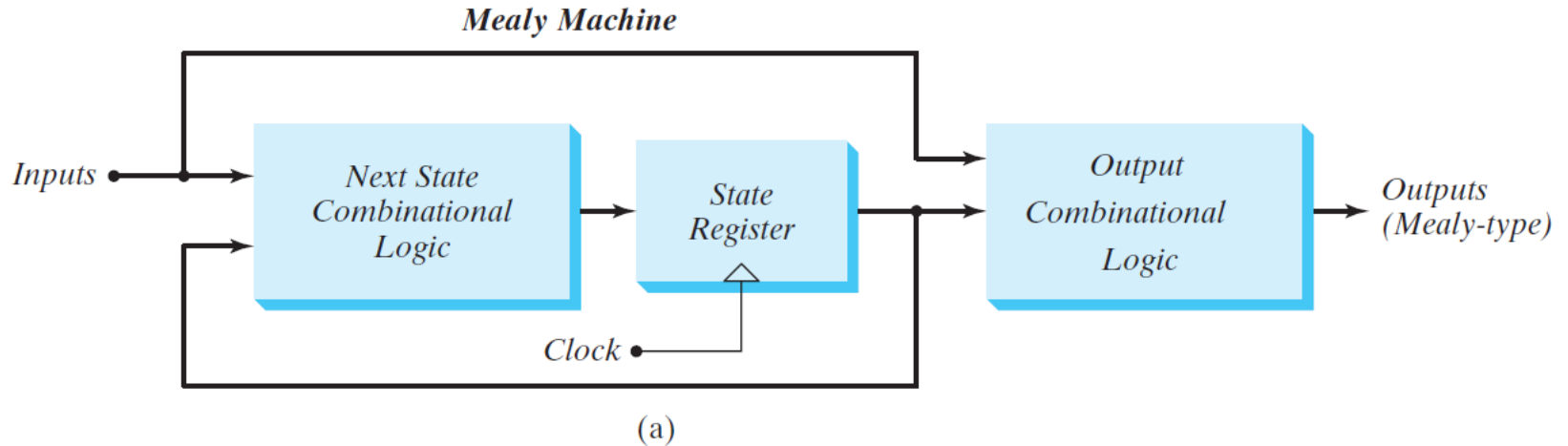


Block diagrams of Mealy and Moore state machines


# Mealy FSM

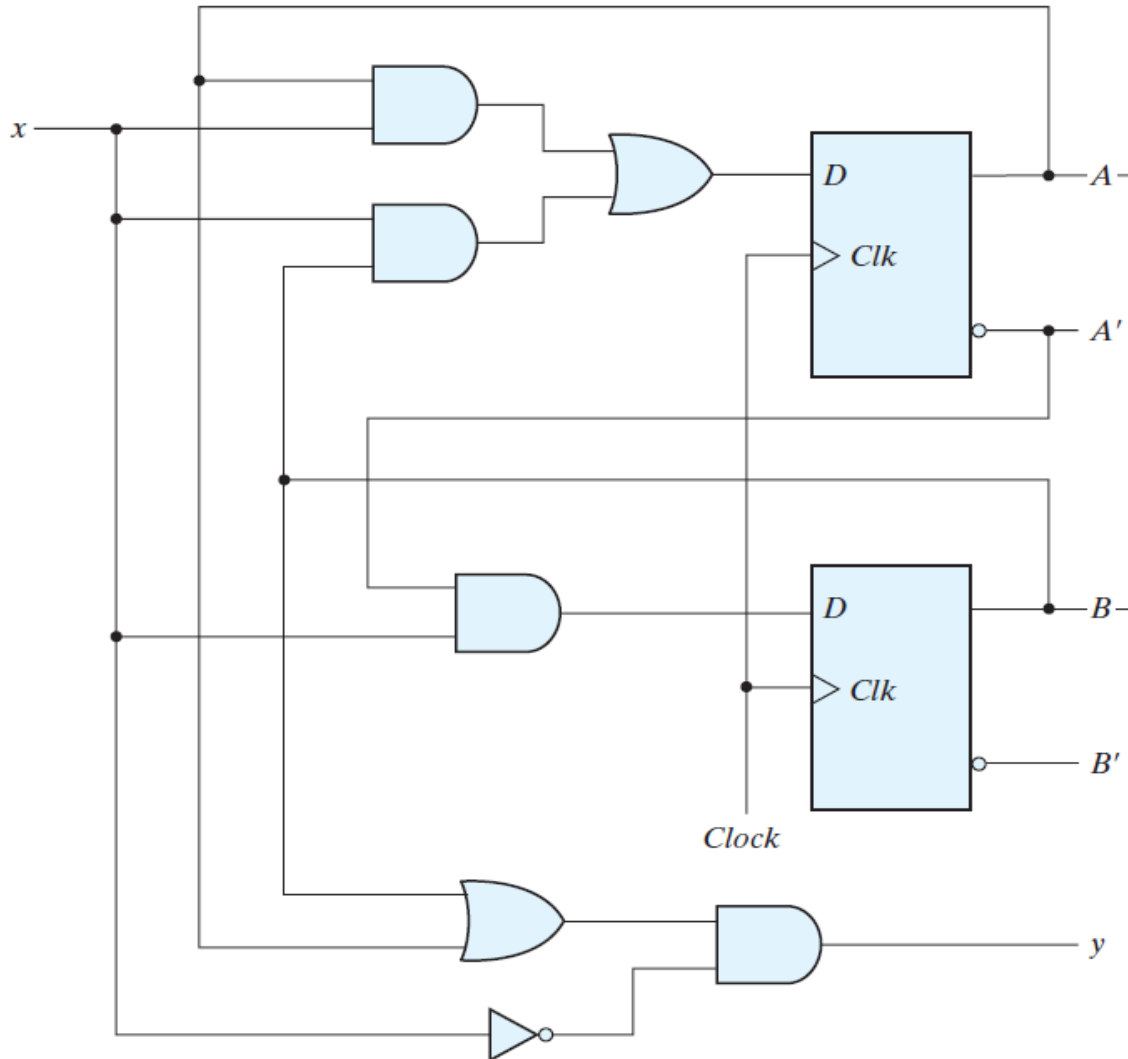


# Mealy FSM

 


# Moore FSM

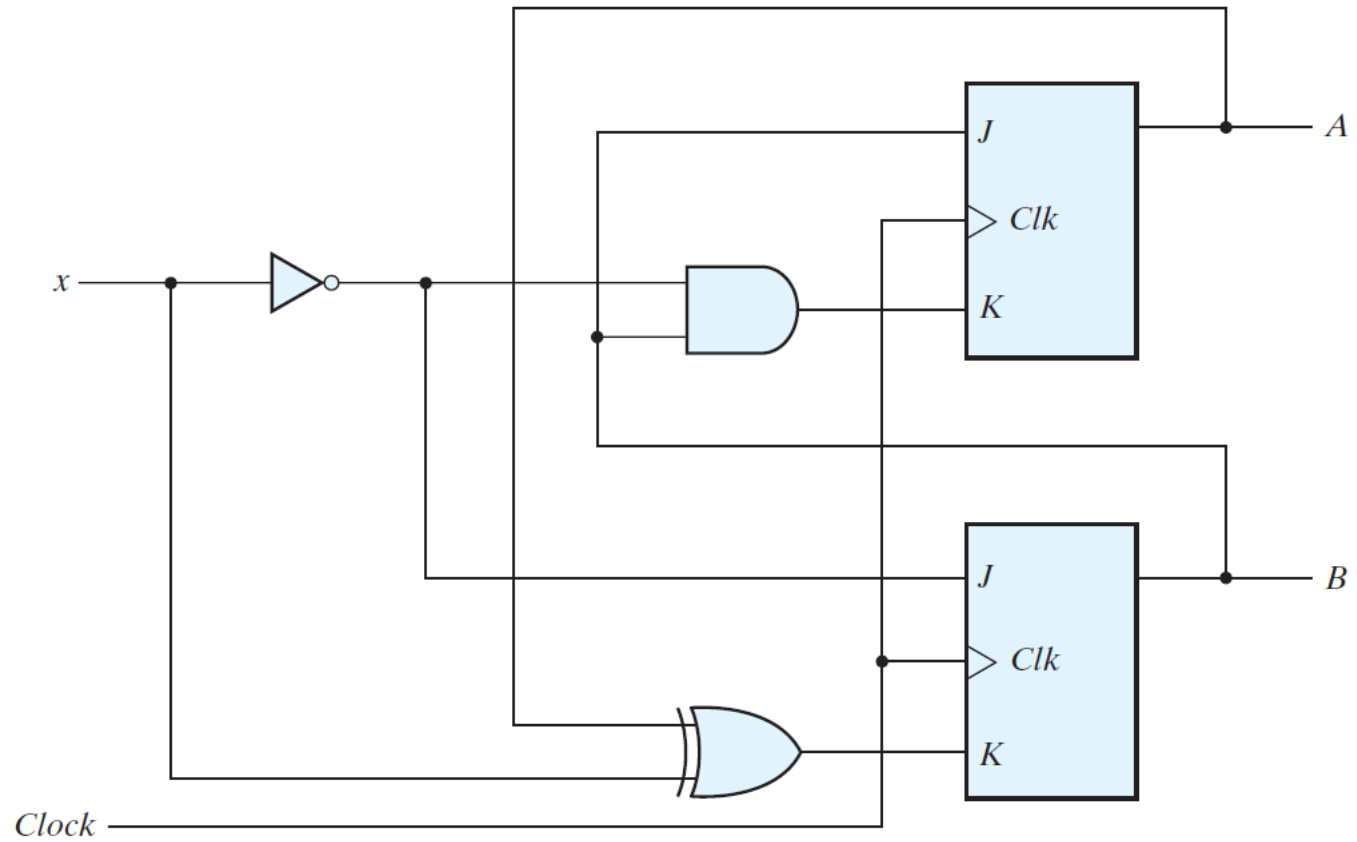


# Moore FSM

 

# Moore FSM

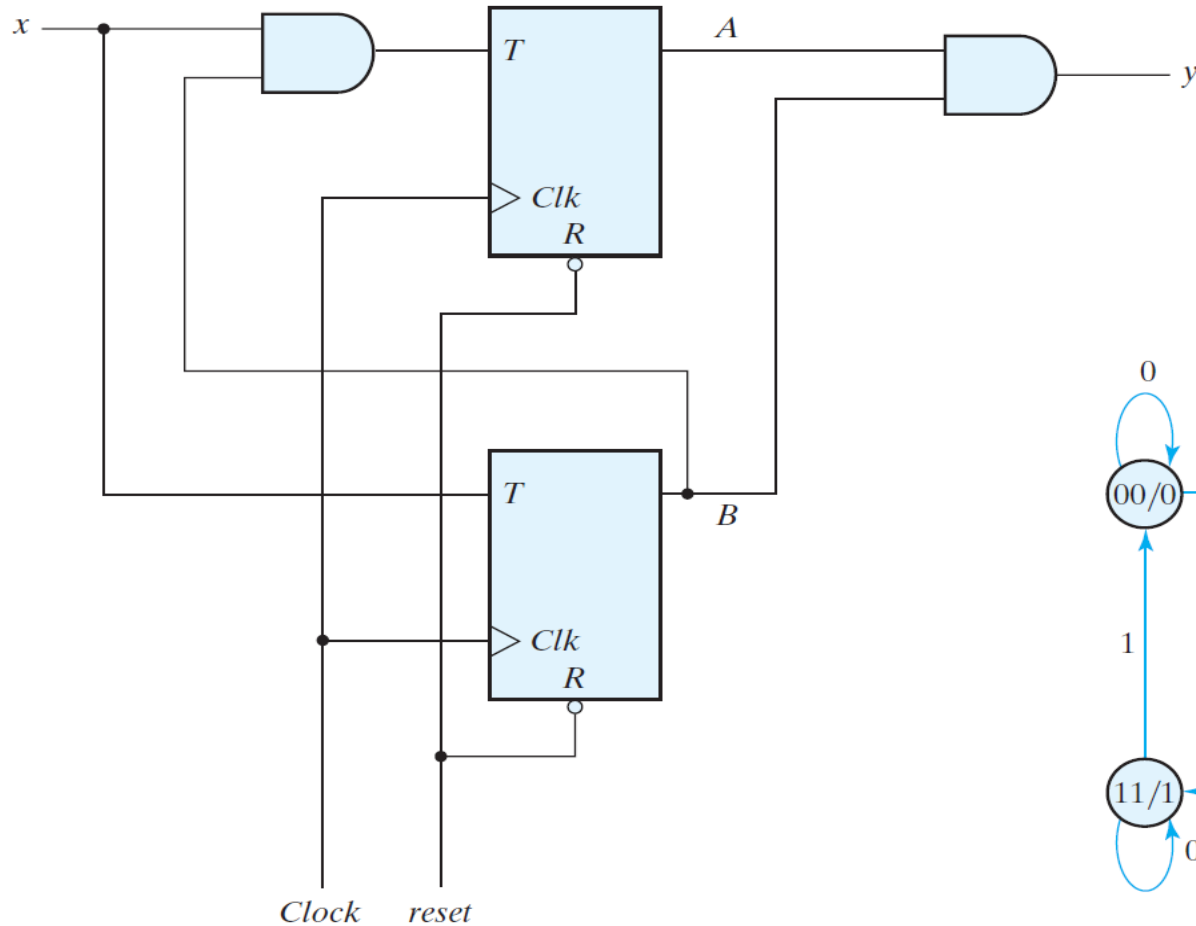

(a) Circuit diagram

 

(b) State diagram


# State reduction



# State reduction


- Reduction in number of flip-flops in a sequential circuit – state reduction.
- Reduces the number of states from a state table – keeping the external input output requirements unchanged.

# State reduction procedure - example

 

# State reduction procedure - example

state	<i>a</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>f</i>	<i>g</i>	<i>f</i>	<i>g</i>	<i>a</i>
input	0	1	0	1	0	1	1	0	1	0	0	
output	0	0	0	0	0	1	1	0	1	0	0	

 

# State reduction procedure - example

state	<i>a</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>f</i>	<i>g</i>	<i>f</i>	<i>g</i>	<i>a</i>
input	0	1	0	1	0	1	1	0	1	0	0	
output	0	0	0	0	0	1	1	0	1	0	0	

- Output and state sequence for a given input sequence.
- Top of the next column – indicates next state.
- Problem of state reduction – finding ways to reduce the number of states in a sequential circuit without altering input/output relationships.

# State reduction procedure - example

<b>state</b>	<i>a</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>f</i>	<i>g</i>	<i>f</i>	<i>g</i>	<i>a</i>
input	0	1	0	1	0	1	1	0	1	0	0	
output	0	0	0	0	0	1	1	0	1	0	0	

*State Table*

<b>Present State</b>	<b>Next State</b>		<b>Output</b>	
	<i>x</i> = 0	<i>x</i> = 1	<i>x</i> = 0	<i>x</i> = 1
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

# State reduction procedure - example

- “Two states are said to be equivalent if, for each member of the set of inputs, they give exactly the same output and send the circuit either to the same state or to an equivalent state.”
- When two states are equivalent, one of them can be removed without altering the input–output relationships.

# State reduction procedure - example

*State Table*

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

- *e* and *g* – same next state , same output for both input combinations.
- *g* and *e* – equivalent states.

# State reduction procedure - example

## *Reducing the State Table*

<b>Present State</b>	<b>Next State</b>		<b>Output</b>	
	<b><math>x = 0</math></b>	<b><math>x = 1</math></b>	<b><math>x = 0</math></b>	<b><math>x = 1</math></b>
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>e</i>	<i>f</i>	0	1

- Row with present state *g* removed
- State *g* – replaced with state *e* each time it occurs in next state column.




# State reduction procedure - example

*Reduced State Table*

<b>Present State</b>	<b>Next State</b>		<b>Output</b>	
	<b><math>x = 0</math></b>	<b><math>x = 1</math></b>	<b><math>x = 0</math></b>	<b><math>x = 1</math></b>
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1

Final reduced state table – 5 states.

# State reduction procedure - example

 

Final reduced state diagram

# Design procedure for sequential circuits

- Design starts from set of specifications – logic diagram or a list of Boolean functions.
- Truth table – combinational circuit, state table – sequential circuit.
- Design specification – state table or state diagram – choose the flip-flops + required combinational circuits.
- No.of flip-flops – no. of states needed.
- Derive Combinational circuit – by the evaluation of flip-flop input –output equations.

# Design procedure for sequential circuits

1. From the word description and specifications of the desired operation, derive a state diagram for the circuit.
2. Reduce the number of states if necessary.
3. Assign binary values to the states.
4. Obtain the binary-coded state table.
5. Choose the type of flip-flops to be used.
6. Derive the simplified flip-flop input equations and output equations.
7. Draw the logic diagram.


# Design procedure for sequential circuits

- Logic synthesis tools (software) – develop HDL description from state diagram.
- Synthesis tools – determine the circuit elements and structure – implements the description.
- Automated synthesis tools in industries – designing massive integrated circuits.

# State diagram from word specification - example

Design a circuit that detects a sequence of three or more consecutive 1's in a string of bits coming through an input line..
 
# State diagram from word specification - example



# State diagram from word specification - example


State diagram – HDL tools – manual design.

Next step – state table – state assignment.

Four states – two binary variables – implement the design with D flip-flops.



 
# State diagram from word specification - example




*State Table for Sequence Detector*

Present State		Input $x$	Next State		Output $y$
$A$	$B$		$A$	$B$	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

 
# State diagram from word specification - example



$$D_A = Ax + Bx$$

 


$$D_B = Ax + B'x$$

 

$$y = AB$$

**K-Maps for sequence detector**
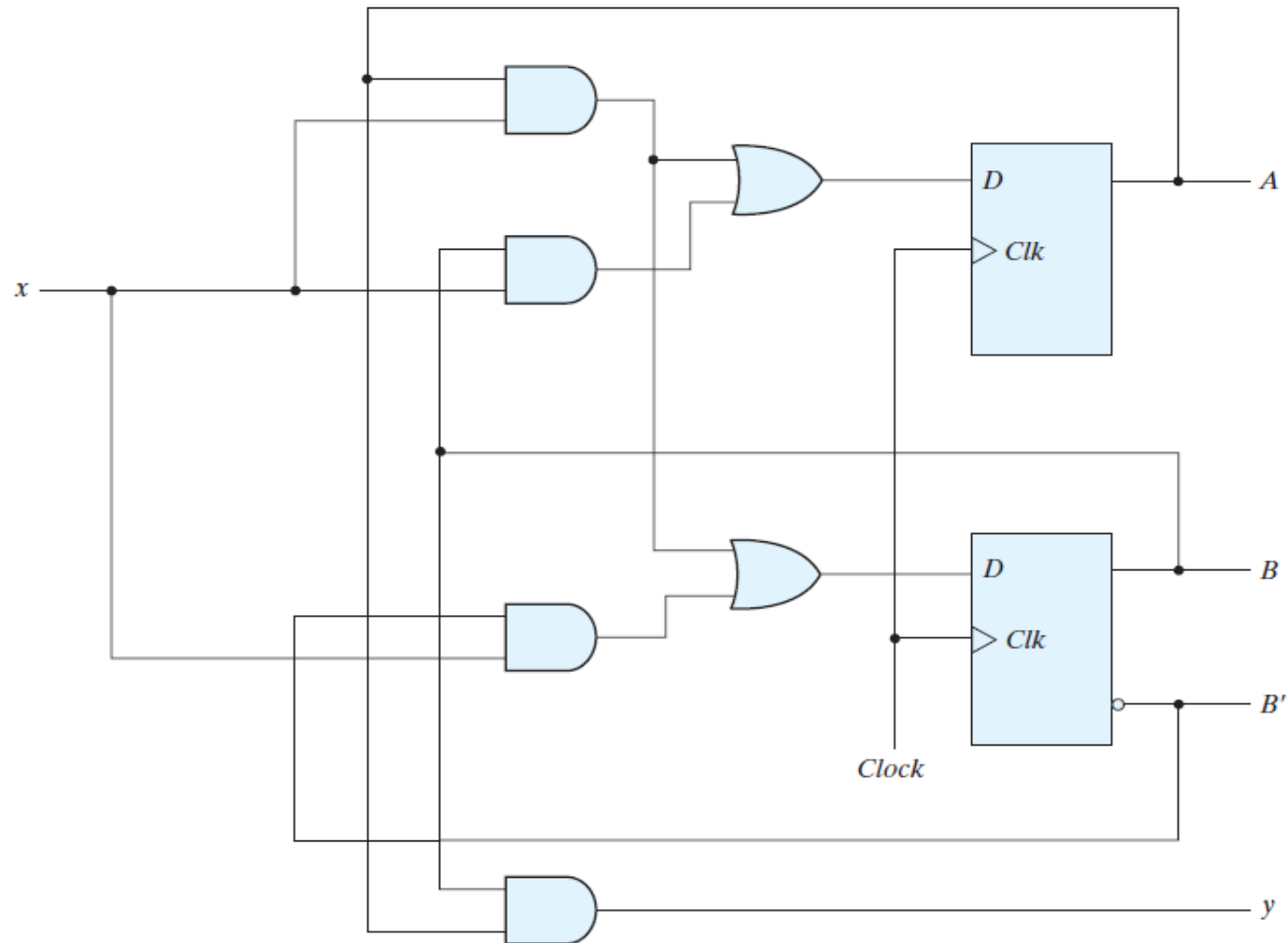
# State diagram from word specification - example



# Flip-flop characteristic table

## *Flip-Flop Characteristic Tables*

### **JK Flip-Flop**

<b><i>J</i></b>	<b><i>K</i></b>	<b><math>Q(t + 1)</math></b>	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

### **D Flip-Flop**

<b><i>D</i></b>	<b><math>Q(t + 1)</math></b>	
0	0	Reset
1	1	Set

### **T Flip-Flop**

<b><i>T</i></b>	<b><math>Q(t + 1)</math></b>	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

# Flip-flop excitation table

- Characteristic table useful - analyzing the next state when the present state and input known.
- In design process – present state to next state transition is known – need to identify the flip-flop input conditions making required transition.

## *Flip-Flop Excitation Tables*

$Q(t)$	$Q(t = 1)$	$J$	$K$
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

(a)  $JK$  Flip-Flop

$Q(t)$	$Q(t = 1)$	$T$
0	0	0
0	1	1
1	0	1
1	1	0

(b)  $T$  Flip-Flop

# Design with JK flip-flop

*State Table and JK Flip-Flop Inputs*

<b>Present State</b>		<b>Input</b>	<b>Next State</b>	
<b>A</b>	<b>B</b>		<b>A</b>	<b>B</b>
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

# Design with JK flip-flop

## State Table and JK Flip-Flop Inputs

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

# Design with JK flip-flop

		$B$			
		$Bx$	00	01	11
$A$	0	$m_0$	$m_1$	$m_3$	$m_2$ 1
	1	$m_4$ X	$m_5$ X	$m_7$ X	$m_6$ X
		$x$			

$J_A = Bx'$

		$B$			
		$Bx$	00	01	11
$A$	0	$m_0$ X	$m_1$ X	$m_3$ X	$m_2$ X
	1	$m_4$	$m_5$	$m_7$ 1	$m_6$
		$x$			

$K_A = Bx$

		$B$			
		$Bx$	00	01	11
$A$	0	$m_0$	$m_1$ 1	$m_3$ X	$m_2$ X
	1 <td><math>m_4</math></td> <td><math>m_5</math> 1</td> <td><math>m_2</math> X</td> <td><math>m_6</math> X</td>	$m_4$	$m_5$ 1	$m_2$ X	$m_6$ X
		$x$			

$J_B = x$


		$B$			
		$Bx$	00	01	11
$A$	0	$m_0$ X	$m_1$ X	$m_3$	$m_2$ 1
	1	$m_4$ X	$m_5$ X	$m_7$ 1	$m_6$
		$x$			

$K_B = (A \oplus x)'$

Maps for  $J$  and  $K$  input equations




# Design with JK flip-flop

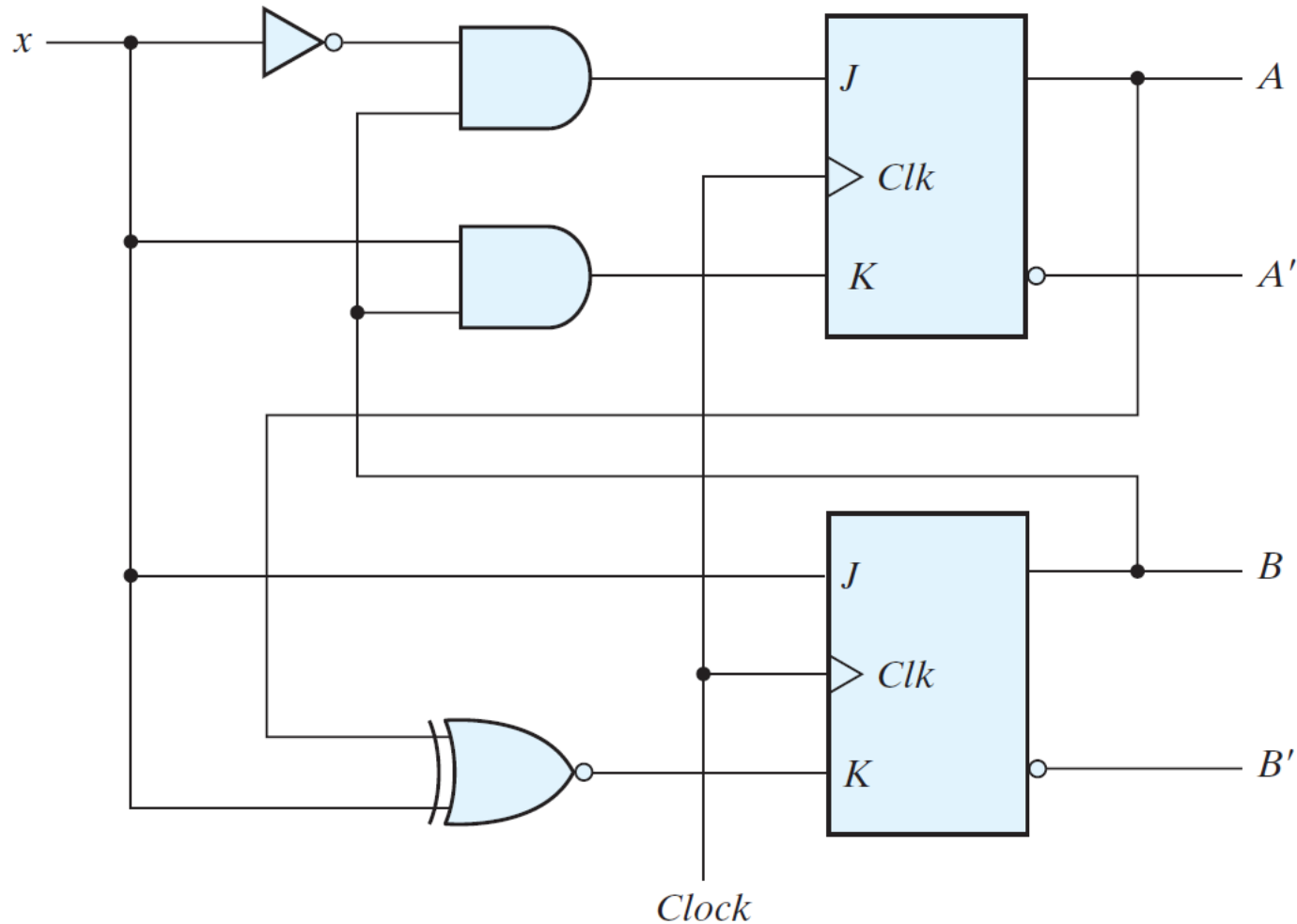

Logic diagram for sequential circuit with JK flip-flops

# Design with T flip-flop

 


**State diagram of three-bit binary counter**

# Design with T flip-flop

*State Table for Three-Bit Counter*


Present State			Next State			Flip-Flop Inputs		
$A_2$	$A_1$	$A_0$	$A_2$	$A_1$	$A_0$	$T_{A2}$	$T_{A1}$	$T_{A0}$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1

# Design with T flip-flop

 

Maps for three-bit binary counter

# Design with T flip-flop

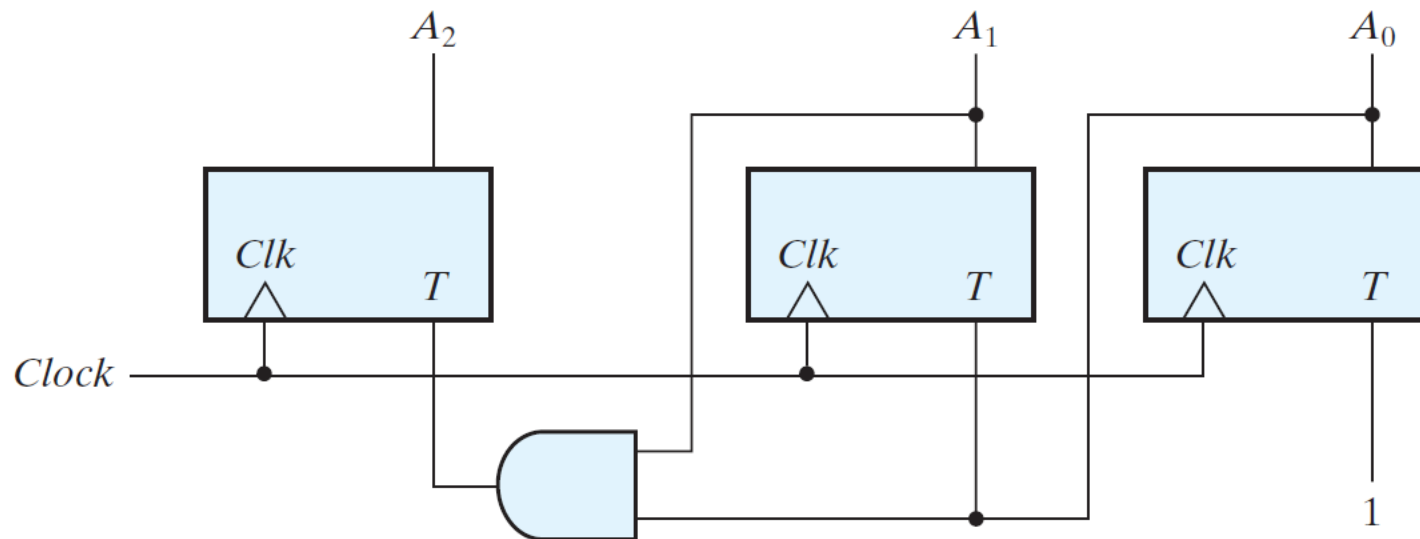


Logic diagram of three-bit binary counter

# Timing diagrams

- Timing relationship between the inputs, outputs and clock for sequential circuits.
- Timing diagrams important –sequential circuits used as a part of larger digital system.
- State change always occurs – in response to active clock edge.
- Circuit output change – at the time of flip-flops state change / input change – depends the type

# Parity checker

 

Block Diagram  
for Parity Checker

One input, clock  
Serial data coming  
in(data enters the  
circuit sequentially

7 Data Bits							Parity Bits
0	0	0	0	0	0	0	1
0	0	0	0	0	0	1	0
0	1	1	0	1	1	0	1
1	0	1	0	1	0	1	1
0	1	1	1	0	0	0	0
8-Bit Word							


Example Of 8 bit  
words with odd  
parity

# Parity checker


- One input, clock
- Serial data coming in (data enters the circuit sequentially – one bit at a time.)
- Sequence of 0's and 1's applied to the X input.
- Output  $Z = 1$ , if the total number of 1 inputs received odd – i.e – input parity odd.
- Output  $Z = 0$ , error in transmission, total no. of one received is even.



# Parity checker

 

Block Diagram  
for Parity Checker

 

State Graph for  
Parity Checker

# Parity checker


(a)

Present State	Next State		Present Output
	$X = 0$	$X = 1$	
$S_0$	$S_0$	$S_1$	0
$S_1$	$S_1$	$S_0$	1

(b)


$Q$	$Q^+$		$T$		$Z$
	$X = 0$	$X = 1$	$X = 0$	$X = 1$	
0	0	1	0	1	0
1	1	0	0	1	1

State Table for Parity Checker

 


Parity Checker

# Parity checker

 

Waveforms for  
Parity Checker

# Moore sequential circuit

 

# Timing diagrams

- X input synchronized with clock. Initial state  $A = B = 0$
- State change occurs after the rising edge of the clock.
- $Z = A \text{ EX-OR } B$ .
- $X = 0$   $D_A = 1$  and  $D_B = 0$
- Next state  $A = 1, B = 1$  , after first rising edge of the clock.

# Timing diagrams

- $X = 01101$
- $A = 0, B = 0, X = 0, Z = 0, D_A = 1$  and  $D_B = 0$
- $A = 1, B = 0, X = 1, Z = 1, D_A = 0$  and  $D_B = 1$
- $A = 0, B = 1, X = 1, Z = 1, D_A = 1$  and  $D_B = 1$
- $A = 1, B = 1, X = 0, Z = 0, D_A = 0$  and  $D_B = 1$
- $A = 0, B = 1, X = 1, Z = 1, D_A = 1$  and  $D_B = 1$
- $A = 1, B = 1$

# Timing diagrams


$$X = \quad 0 \quad 1 \quad 1 \quad 0 \quad 1$$

$$A = \quad 0 \quad 1 \quad 0 \quad 1 \quad 0 \quad 1$$

$$B = \quad 0 \quad 0 \quad 1 \quad 1 \quad 1 \quad 1$$

$$Z = (0) \quad 1 \quad 1 \quad 0 \quad 1 \quad 0$$


# Moore sequential circuit

 

Timing Chart



# Mealy sequential circuit

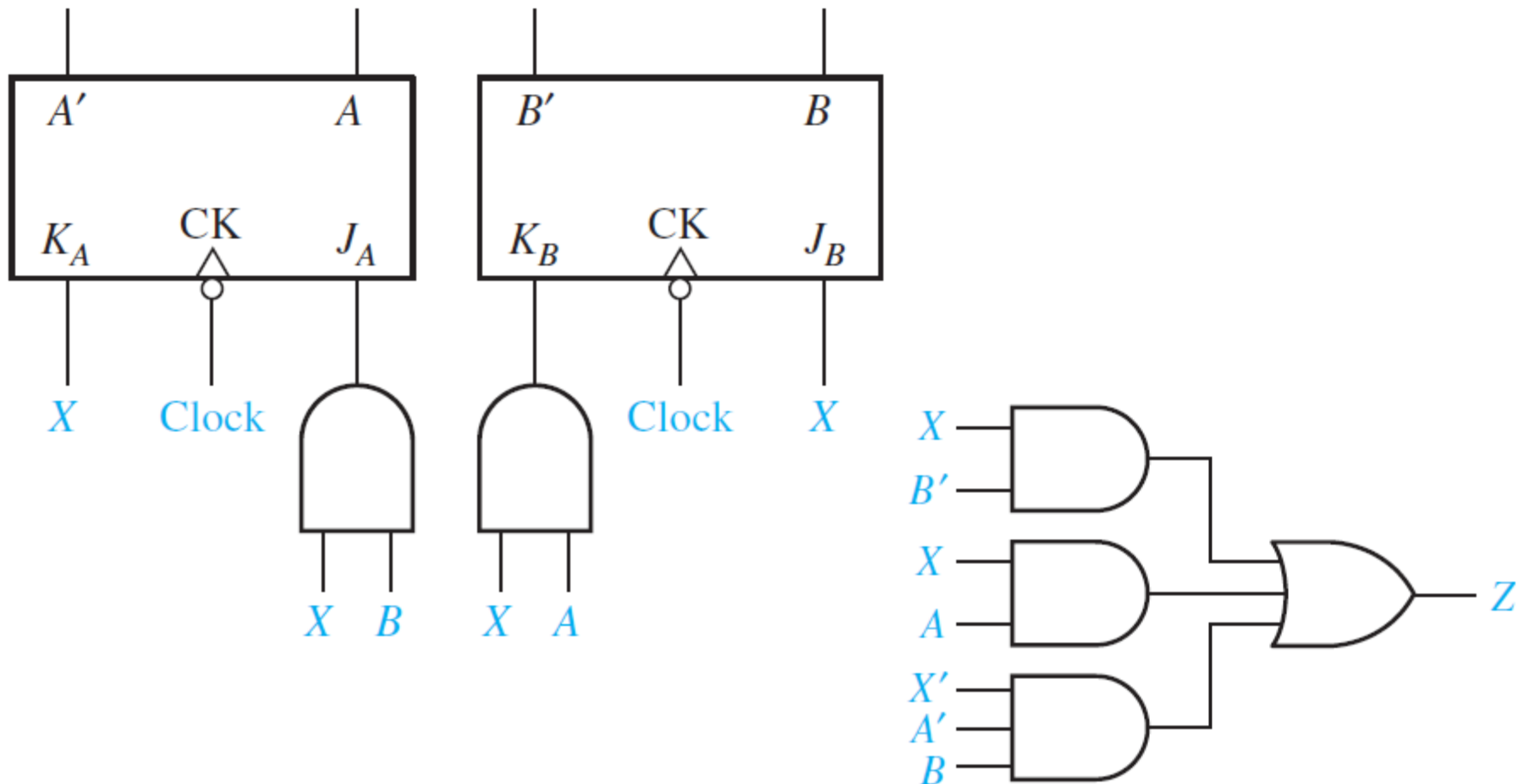

# Mealy sequential circuit


$$X = 1 \quad 0 \quad 1 \quad 0 \quad 1$$

$$A = 0 \quad 0 \quad 0 \quad 1 \quad 1 \quad 0$$

$$B = 0 \quad 1 \quad 1 \quad 1 \quad 1 \quad 0$$

$$Z = 1(0) \ 1 \quad 0(1) \ 0 \quad 1 \quad \text{(False outputs are indicated in parentheses.)}$$

# Mealy sequential circuit

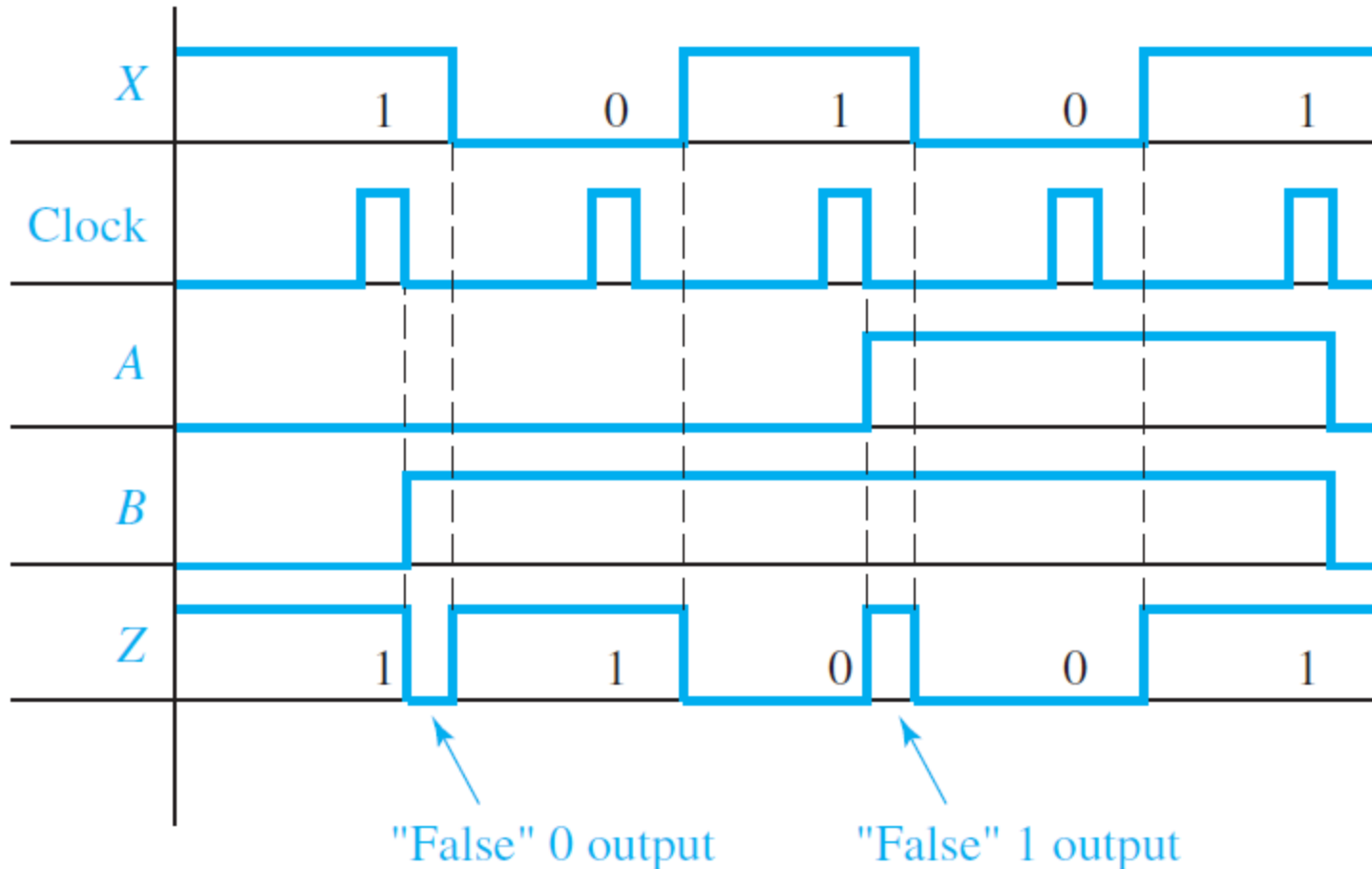

# Timing diagrams

- Necessary to interpret the output waveform carefully in a Mealy circuit.
- After change in circuit state – before change in input – output temporarily assume an incorrect value – false output.
- False value – circuit changed to new state, but old input associated with the previous state is still present.

# Timing diagrams

- Mealy circuit output – only of interest immediately proceeding the active clock edge.
- Extra output changes might occur between active clock edges – should be ignored.
- False outputs – glitches and spikes.
- State change – output change – input has not changed to new value – output value may not be correct – results in false output or glitch.
- Ignoring the false outputs –  $Z = 11001$

# Timing diagrams

- Moore circuit – output change only when the flip flop changes state – which is synchronized with the clock – no false outputs or glitches in a Moore circuit.
- Displacement of output sequence w.r.t input sequence – Moore circuit.

# Interpretation of timing charts


When constructing timing charts, note that a state change can only occur after the rising (or falling) edge of the clock, depending on the type of flip-flop used.

The input will normally be stable immediately before and after the active clock edge.

For a Moore circuit, the output can change only when the state changes, but for a Mealy circuit, the output can change when the input changes as well as when the state changes. A false output may occur between the time the state changes and the time the input is changed to its new value. (In other words, if the state has changed to its next value, but the old input is still present, the output may be temporarily incorrect.)

For Mealy circuits, the best time to read the output is just before the active edge of the clock, because the output should always be correct at that time.


# Timing diagrams

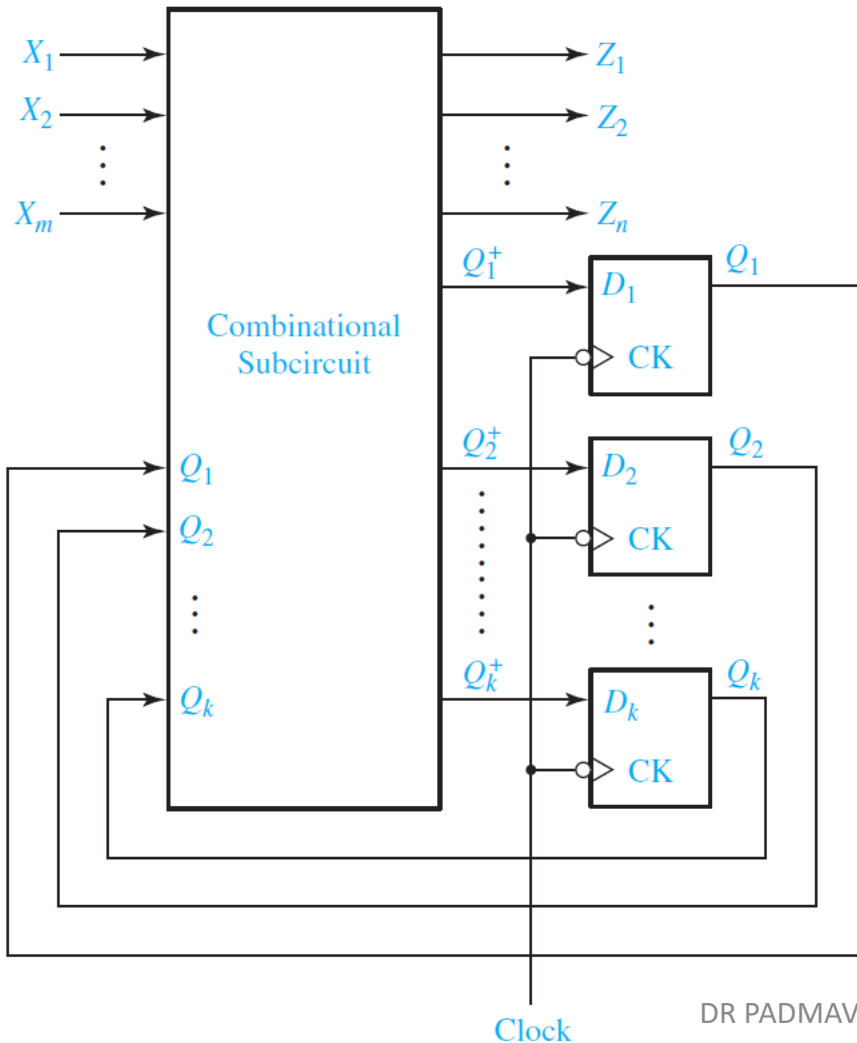

General Model  
for Mealy Circuit  
Using Clocked  
D Flip-Flops





# Timing diagrams



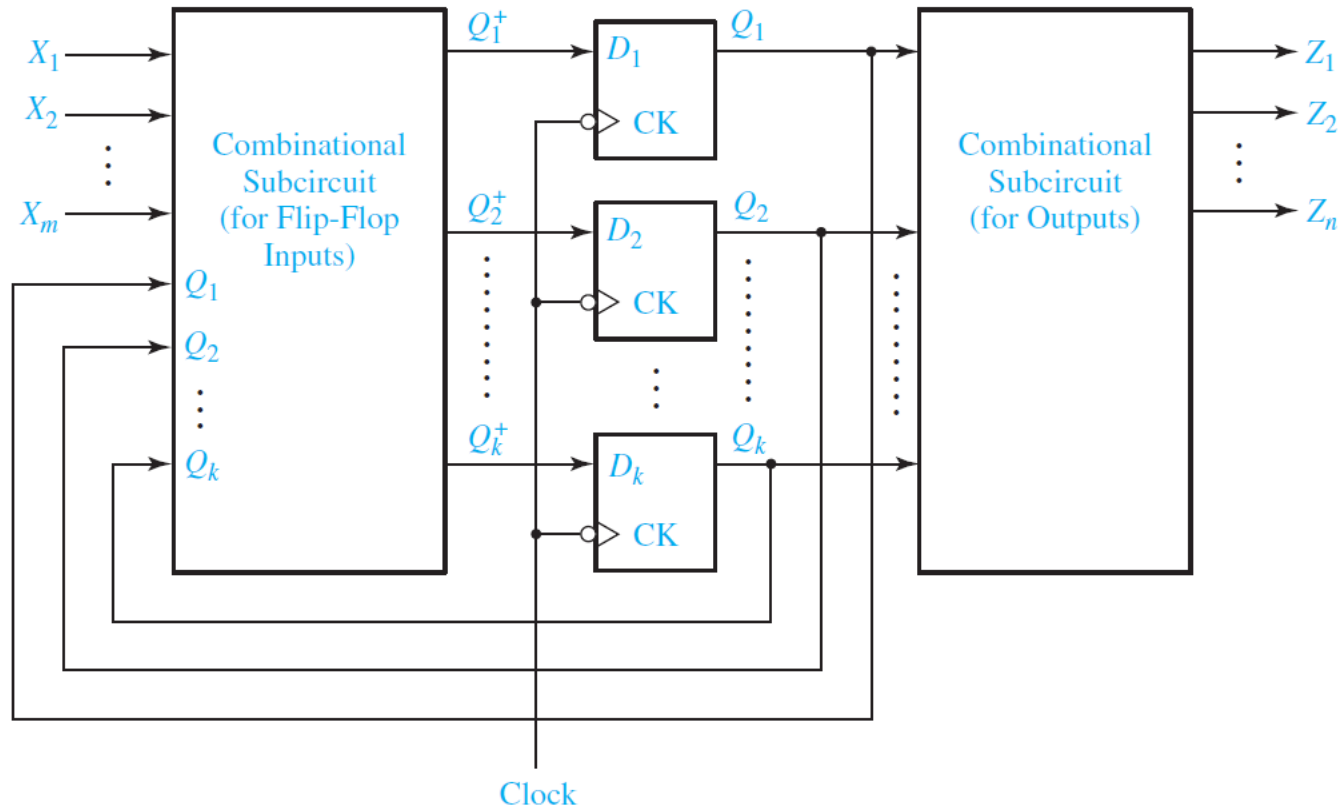


General Model  
for Moore Circuit  
Using Clocked  
D Flip-Flops

  
# State table and state diagram – practice problem - 1



  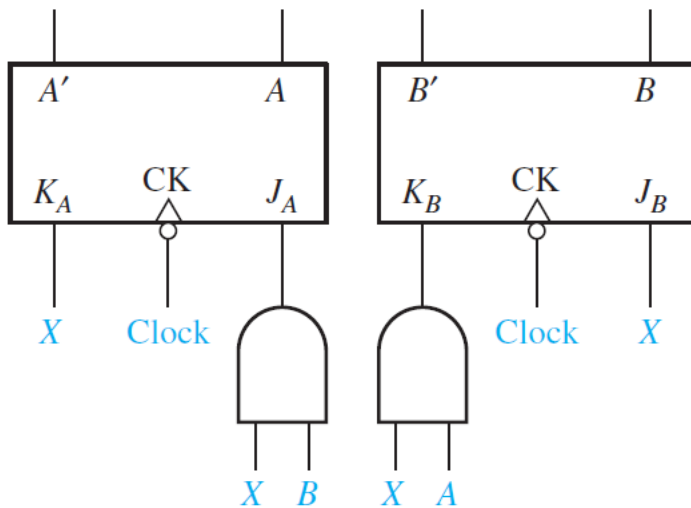
# State table and state diagram – practice problem - 2


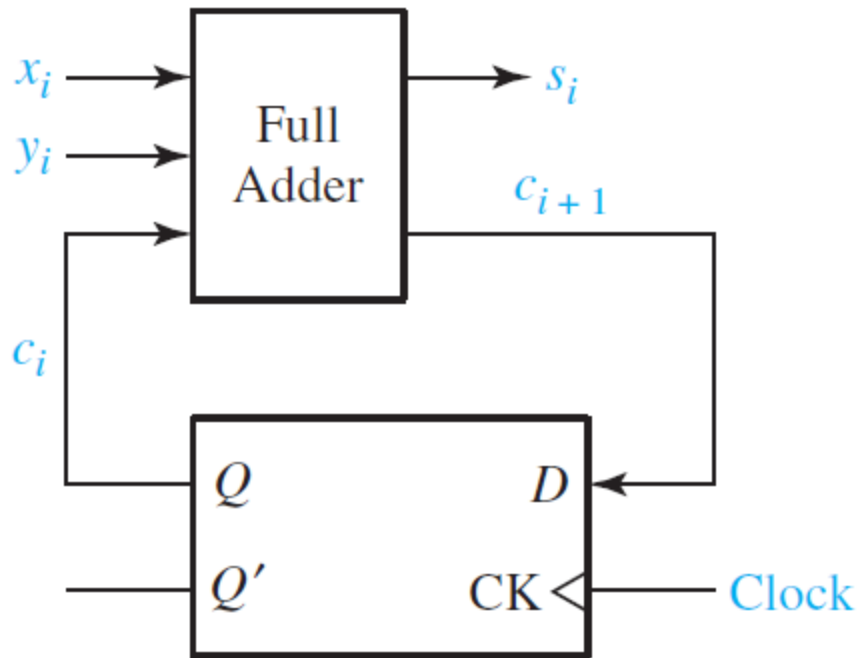
# State table and state diagram – practice problem - 3




$x_i$	$y_i$	$c_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


# State table and state diagram – practice problem - 4

Present State	Next State				Present Output ( $Z_1Z_2$ )			
	$X_1 X_2 = 00$	01	10	11	$X_1X_2 = 00$	01	10	11
$S_0$	$S_3$	$S_2$	$S_1$	$S_0$	00	10	11	01
$S_1$	$S_0$	$S_1$	$S_2$	$S_3$	10	10	11	11
$S_2$	$S_3$	$S_0$	$S_1$	$S_1$	00	10	11	01
$S_3$	$S_2$	$S_2$	$S_1$	$S_0$	00	00	01	01

 
State table with multiple  
input and output





# Timing chart – example

 

# Timing chart – example

 

Initial values are shown.

 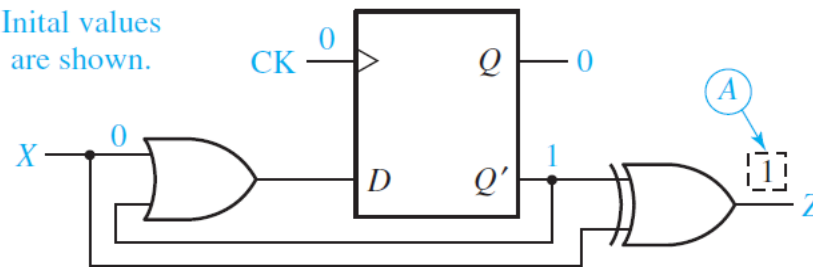

DR PADMAVATHI, NITK  
Initial values of X and Z are shown in shaded area (before rising edge of clock).

# Timing diagrams

- Each time input X changes, trace the changes on the state graph, state table, the circuit and the timing chart.



# Timing diagrams

- Several changes in input – affects output as well.
- Input must assume correct value before the rising edge of the clock – output should be read at this time (D).
- After rising edge of the clock – no state change – no output change.
- Input changes to new value – output change to its new value (F) – should be read before the next rising clock edge.

# Timing diagrams

- Input and output sequence before each rising edge of the clock

$$X = 0 \ 1 \ 0$$

$$Z = 1 \ 1 \ 0$$

- Verify this in state table, state graph and state diagram.