

Review of logic design fundamentals

K-map – map entered variables

- Functions – more than 5 variables – simplification using map entered variables.

A	B	C	D	E	F	G
0	0	0	0	X	X	1
0	0	0	1	X	X	X
0	0	1	0	X	X	1
0	0	1	1	X	X	1
0	1	0	1	1	X	1
0	1	1	1	1	X	1
1	0	0	1	X	1	1
1	0	1	0	X	X	X
1	0	1	1	X	X	1
1	1	0	1	X	X	X
1	1	1	1	X	X	1

- Partial truth table for a 6 variable function
- Unspecified combinations – output = 0.

K-map – map entered variables

- E and F are input variables with greatest number of don't cares.
- K map - formed with A, B,C ,D - remaining two variables entered inside the map.
- E appears in a square $E = 1$ – corresponding minterm is present in the function G.
- F appears in a square $F = 1$.

K-map – map entered variables

AB		CD				AB		CD				AB		CD				AB		CD			
		00	01	11	10			00	01	11	10			00	01	11	10			00	01	11	10
00		1				00		1				00		X				00		X			
01		X	E	X	F	01		X			X			X	1	X		01		X		X	1
11		1	E	1	1	11		1			1	1		X	1	X	X	11		X		X	X
10		1			X	10		1					X	X			X	10		X			X

G

$E = F = 0$
 $MS_0 = A'B' + ACD$

$E = 1, F = 0$
 $MS_1 = A'D$

$E = 0, F = 1$
 $MS_2 = AD$

Simplification using map entered variables

$$G = A'B' + ACD + EA'D + FAD$$

K-map – map entered variables

$$F = MS_0 + P_1MS_1 + P_2MS_2 + \dots$$

where

- MS_0 is the minimum sum obtained by setting $P_1 = P_2 = \dots = 0$.
- MS_1 is the minimum sum obtained by setting $P_1 = 1, P_j = 0 (j \neq 1)$, and replacing all 1s on the map with don't cares.
- MS_2 is the minimum sum obtained by setting $P_2 = 1, P_j = 0 (j \neq 2)$, and replacing all 1s on the map with don't cares.


$$G = A'B' + ACD + EA'D + FAD$$

Design with NAND and NOR gates


- Concept of universality: Gates which can implement any Boolean function without the need to use any other types of gates.
- NAND and NOR universal gates.
- Use NAND and NOR alone to implement the basic gates.

Design with NAND and NOR gates


NOT or **INV**

 

AND

 


OR

 

Design with NAND and NOR gates

NAND:

 

NOR:



Implementation of NAND and NOR easier than that of AND and OR gates.

Bubble – complement.

Design with NAND and NOR gates

AND – NAND - adding an inversion bubble at the output.


OR – NAND – adding inversion bubble at the inputs.

Inverter output drives inverted input – no further action required.


Non inverted gate output drives an inverted gate input or vice versa – insert an inverter.

Variable drives inverted input - complement the variable.


Design with NAND and NOR gates

 

(a) AND-OR circuit

 

(b) First step in NAND conversion

 

(c) Completed conversion

Conversion of AND-OR circuit to NAND gate

Flip-flops and Latches

Sequential circuits – flip-flops as storage devices.

Types of flip-flops:


D flip-flops

J-K flip-flops

T flip-flops

Flip-flops and Latches

 Clocked D flip-flop with rising edge trigger




D	Q	Q^+
0	0	0
0	1	0
1	0	1
1	1	1

$$Q^+ = D$$

- State change in response to the rising edge of the clock input.
- Q^+ - next state of the Q output after the active edge of the clock.
- D – input before the active edge.

Flip-flops and Latches

J-K flip-flop and its truth table

 


J	K	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q^+ = JQ' + K'Q.$$

- State change occurs following the falling edge of the clock.

Flip-flops and Latches


Clocked T flip-flop

 

$$Q^+ = QT' + Q'T = Q \oplus T$$

- State change occurs following the falling edge of the clock.


Flip-flops and Latches

 

$$Q^+ = S + R'Q.$$

Flip-flops and Latches


S-R latch

 

- Un-clocked flip-flop – SR latch
- Characteristic equation?

Flip-flops and Latches

Transparent D latch

 

G	D	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$Q^+ = GD + G'Q.$$

- No response to input changes unless $G = 1$.
- Level sensitive D flip-flop