

INTRODUCTION TO VERILOG


Synthesis examples

```
assign signal_name = condition ? expression_T : expression_F;
```

```
assign F = E ? A : ( D ? B : C );  
// nested conditional assignment
```

Synthesis examples

 
Cascaded 2 to 1 MUXes using conditional assignment



```
assign F = E ? A : ( D ? B : C );  
// nested conditional assignment
```

Synthesis examples

Cyclic shift register

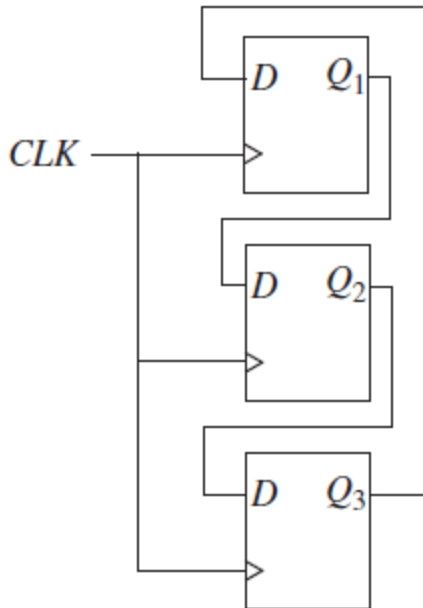

```
always @ (posedge CLK)
begin
    Q1 <= #5 Q3;
    Q2 <= #5 Q1;
    Q3 <= #5 Q2;
end
```

Synthesis examples

At the rising edge of the clock – all of the D inputs loaded into the Flip-flops – state change does not occur until after a propagation delay.

Non-blocking assignment – order of the statements not important.

Synthesis examples

```
module reg3 (Q1,Q2,Q3,A,CLK);  
input      A;  
input      CLK;  
output     Q1,Q2,Q3;  
  
reg        Q1,Q2,Q3;  
  
always @(posedge CLK)  
begin  
    Q3 = Q2;    // statement 1  
    Q2 = Q1;    // statement 2  
    Q1 = A;     // statement 3  
  
end  
  
endmodule
```

Synthesis examples

```
module reg3 (Q1,Q2,Q3,A,CLK);  
  input  A;  
  input  CLK;  
  output Q1,Q2,Q3;  
  reg    Q1,Q2,Q3;  
  always @(posedge CLK)  
  begin  
    Q3 = Q2;    // statement 1  
    Q2 = Q1;    // statement 2  
    Q1 = A;     // statement 3  
  end  
end  
endmodule
```

3 bit shift register.

Blocking operator –
execution of statements
from top to bottom in
order.

Synthesis examples

```
module reg31 (Q1,Q2,Q3,A,CLK);  
  input      A;  
  input      CLK;  
  output     Q1,Q2,Q3;  
  
  reg        Q1,Q2,Q3;  
  
  always @(posedge CLK)  
  begin  
    Q1 = A;    // statement 1  
    Q2 = Q1;   // statement 2  
    Q3 = Q2;   // statement 3  
  
  end  
  
endmodule
```


Synthesis examples

```
module reg31 (Q1,Q2,Q3,A,CLK);
```

Single flip-flop

```
input A;
```

```
input CLK;
```

```
output Q1,Q2,Q3;
```

```
reg Q1,Q2,Q3;
```

```
always @(posedge CLK)
```

```
begin
```

```
    Q1 = A; // statement 1
```


```
    Q2 = Q1; // statement 2
```

```
    Q3 = Q2; // statement 3
```

```
end
```


```
endmodule
```

Synthesis examples

 

1. Verilog code using concurrent statements.
2. Using an always block.

Synthesis examples

 

```
module circuit(A, B, C, D, G);
```

```
input A, B, C, D;
```

```
output G;
```

```
wire E, F;
```


```
assign E = A & & B;
```

```
assign F = E | | C;
```

```
assign G = D & & F;
```

```
endmodule
```

Synthesis examples

 

```
module circuit(A, B, C, D, G);
```

```
input A, B, C, D;
```

```
output reg G;
```

```
reg E, F;
```

```
initial begin
```

```
  E <= 0;
```

```
  F <= 0;
```

```
  G <= 0;
```

```
end
```

```
always @(*)
```

```
begin
```

```
  E <= A & & B;
```

```
  F <= E | | C;
```

```
  G <= F & & D;
```

```
end
```

```
endmodule
```

Writing test bench

- Two types of verification – functional and timing verification.
- Functional verification – study the circuit logical operation independent of timing considerations.
- Timing verification – study the circuit operation, including the effect of delays through the gates.

Writing test bench

Test bench for describing and applying stimulus to an HDL model of the circuit – test and observe its response during simulation.


Test benches – can be quite complex, lengthy.

Care must be taken to –write stimuli that will test a circuit thoroughly

 
Exercise all the operating features that are specified.

Hierarchical modeling concepts

Stimulus block instantiating design block.



Hierarchical modeling concepts

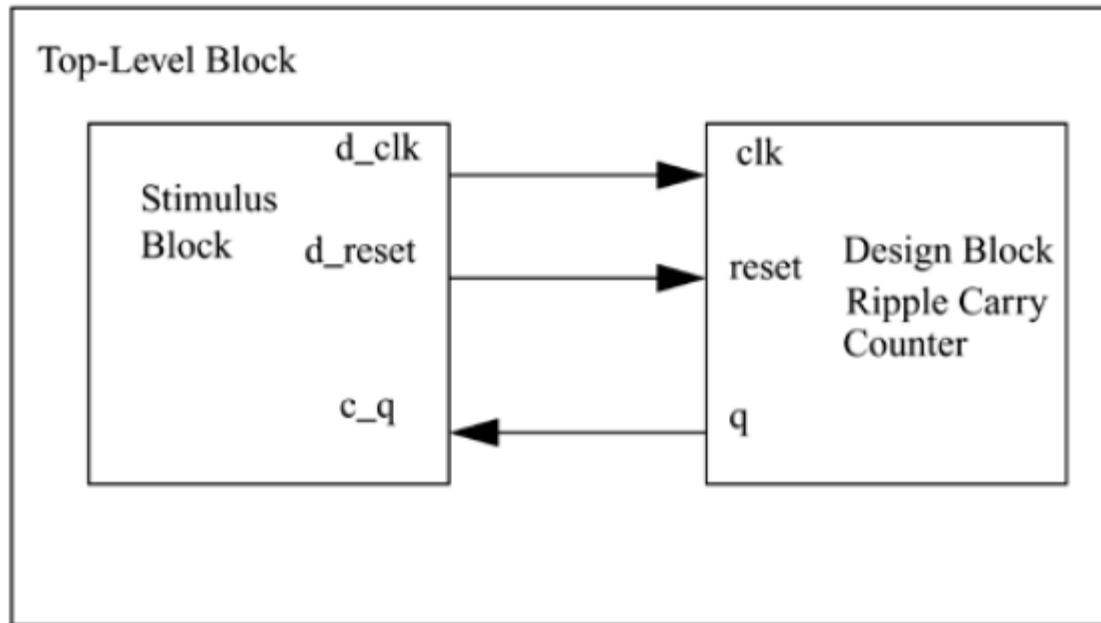

Hierarchical modeling concepts

- Instantiating both the stimulus and design blocks in a top-level dummy module.
- Stimulus block interacts with the design block through interface.
- Top level block simply instantiates the design and stimulus block.

Writing test bench

initial

begin

A = 0; B = 0;

#10 A = 1;

#20 A = 0; B = 1;

end

initial

begin

D = 3'b000;

repeat (7)

#10 D = D + 3'b001;

end

Stimulus test module

```
module test_module_name;
```

```
// Declare local reg and wire identifiers.
```

```
// Instantiate the design module under test.
```

```
// Specify a stopwatch, using $finish to terminate the  
simulation.
```

```
// Generate stimulus, using initial and always statements.
```

```
// Display the output response (text or graphics (or both)).
```

```
endmodule
```

Stimulus test module

- Test module like any other module – but typically has no inputs or outputs.
- Local reg data types, local reg wire types.
- Instantiate the module under test – using local identifiers in the port list.
- Simulator associates the local identifiers within the test bench with the formal identifiers of the module.
- Response to the stimulus – appear in text format as standard output and as waveforms – timing diagrams.

Stimulus test module

- Numerical outputs displayed by system tasks
- Built in system functions – recognized by keywords that begin with \$ symbol.

Some system tasks useful for display:

\$display —display a one-time value of variables or strings with an end-of-line return,

\$write —same as **\$display** , but without going to next line,

\$monitor —display variables whenever a value changes during a simulation run,

\$time —display the simulation time,


\$finish —terminate the simulation.

Stimulus test module

\$display ("%d %b %b", C, A, B);

- Base may be binary, decimal, hexadecimal, or octal - identified with the symbols %b, %d, %h, and %o. (%B, %D, %H, and %O are valid too).
- No commas in the format specification – argument list separated by commas.

Stimulus test module

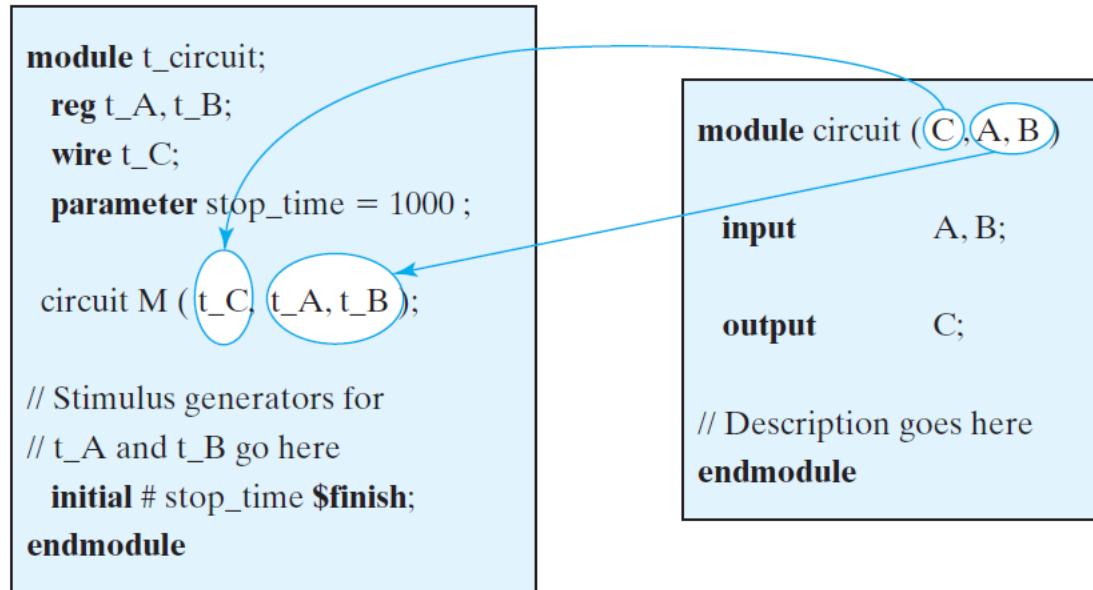

Interaction between stimulus and design modules

Stimulus test module

// Dataflow description of two-to-one-line multiplexer

```
module mux_2x1_df(m_out, A, B, select);
```

```
output m_out;
```

```
input A, B;
```

```
input select;
```

```
assign m_out (select)? A : B;
```

```
endmodule
```


Stimulus test module

// Test bench with stimulus for mux_2x1_df

module t_mux_2x1_df;

wire t_mux_out;

reg t_A, t_B;

reg t_select;

parameter stop_time = 50;

mux_2x1_df M1 (t_mux_out, t_A, t_B, t_select);

// Instantiation of circuit to be tested

initial # stop_time \$finish;

Stimulus test module

```
initial begin                                // Stimulus generator
```

```
t_select = 1; t_A = 0; t_B = 1;
```

```
#10 t_A = 1; t_B = 0;
```

```
#10 t_select = 0;
```

```
#10 t_A = 0; t_B = 1;
```

```
end
```

```
initial begin                                // Response monitor
```

```
// $display (" time Select A B m_out ");
```

```
// $monitor ( $time ,, "%b %b %b %b" , t_select, t_A, t_B,
```

```
t_m_out);
```

Stimulus test module

```
$monitor ( "time = " , $time ,, "select = %b A = %b B =  
%b OUT = %b" , t_select, t_A, t_B, t_mux_out);  
end  
endmodule
```