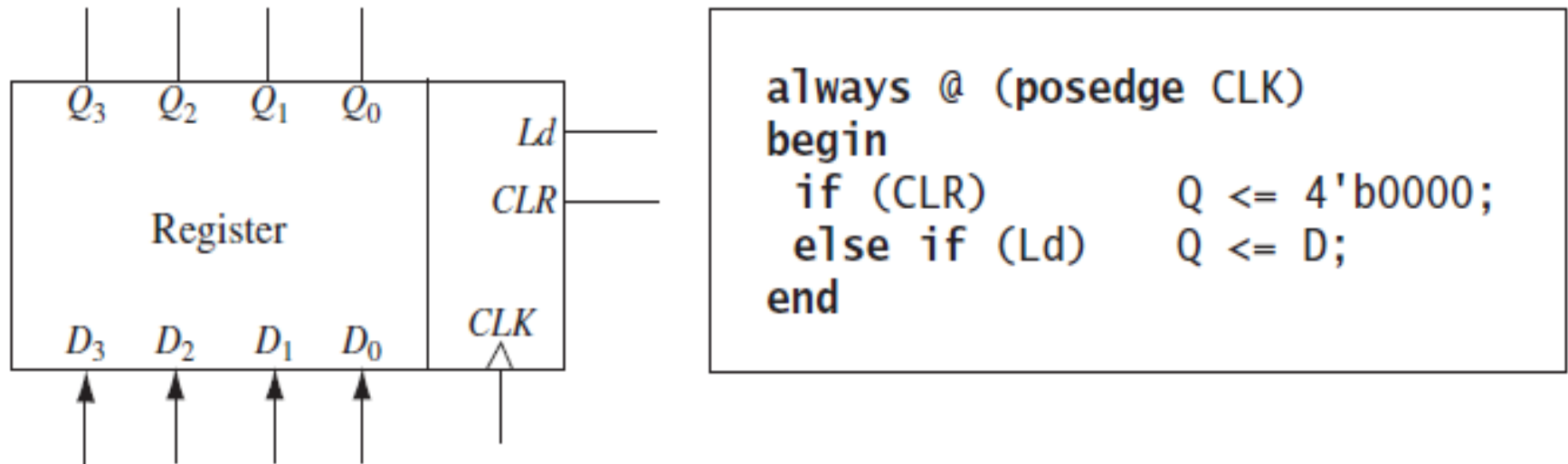



INTRODUCTION TO VERILOG

HDL models of sequential circuits



Register with synchronous clear and load

HDL models of sequential circuits

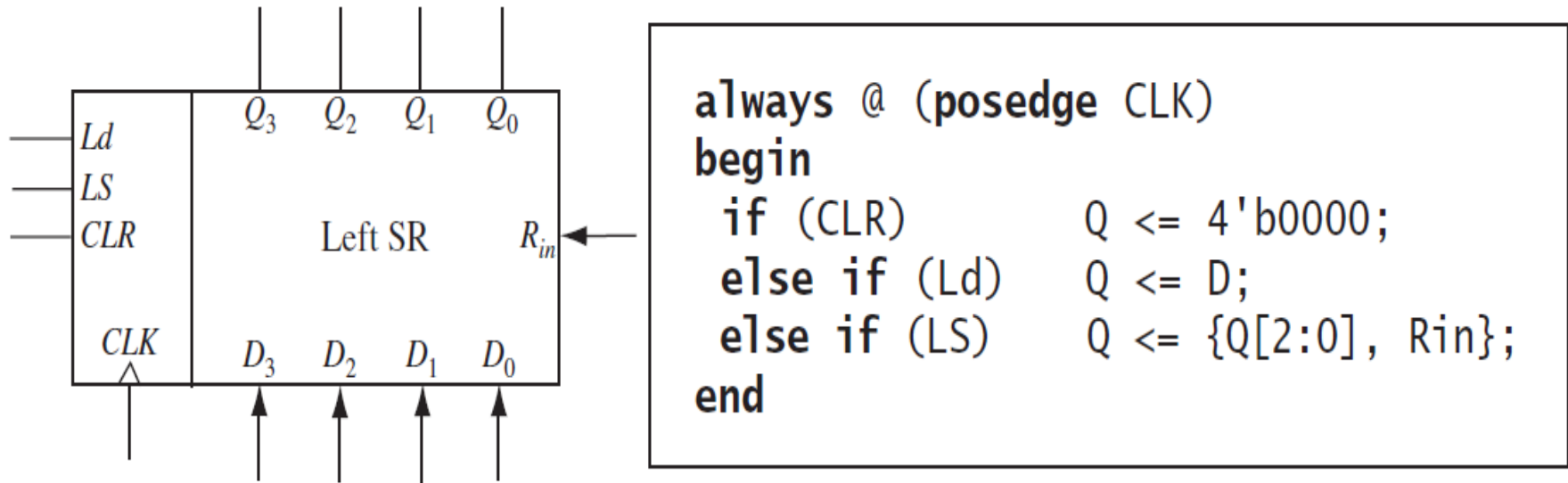

Left shift register with synchronous clear and load

$Q = 1101, Rin = 0$


HDL models of sequential circuits

LS control input

LS = 1, contents of the register shifted left and right most bit set equal to Rin.

Extract right most 3 bits of Q – Q[2:0], concatenate them with Rin. (1010)

HDL models of sequential circuits

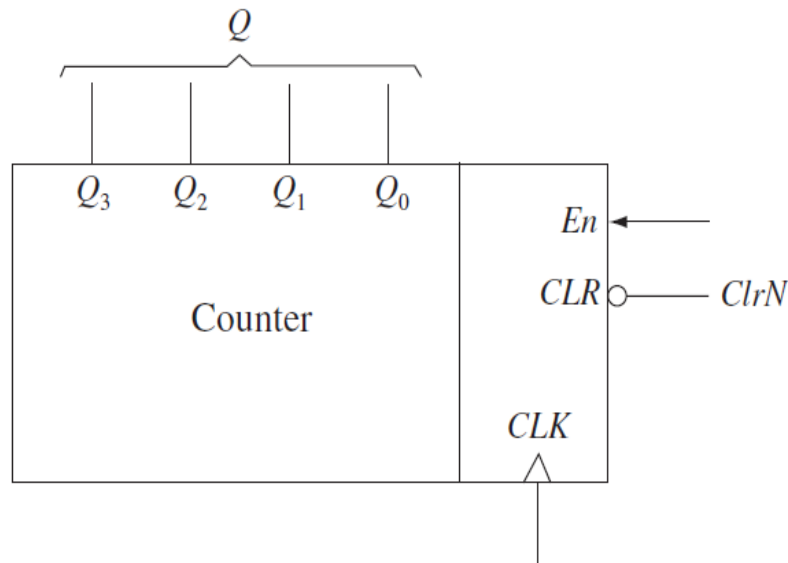

```
reg Q[3:0];  
  
always @ (posedge CLK)  
begin  
    if (~ClrN)    Q <= 4'b0000;  
    else if (En)  Q <= Q + 1;  
end
```

Synchronous counter

HDL models of sequential circuits

```
module counter(clk, CE, reset,  
M, count);
```

```
//CE=Clock Enable, clk=clock,  
M=Mode(up or down)
```

```
input clk, CE, reset, M;  
output [3:0] count;
```

```
reg [3:0] count;
```

```
//reg [<upper>:0] <reg_name>;
```

```
always @(posedge clk)  
    if (reset)  
        count <= 0;  
    else if (CE)  
        if (M)  
            count <= count + 1;  
        else  
            count <= count - 1;  
endmodule
```

HDL models of sequential circuits

```
initial begin
```

```
// Initialize Inputs
```

```
    clk = 0;
```

```
    CE = 0;
```

```
    reset = 1;
```

```
    M = 1;
```

```
#100;
```

```
CE=1;
```

```
#100;
```

```
reset=0;
```

```
#200;
```

```
M=0;
```

```
end
```

```
always #10 clk=~clk;
```

```
endmodule
```

HDL models of sequential circuits

```
force CLK 0 0, 1 100 -repeat 200  
force X 0 0, 1 350, 0 550, 1 750, 0 950, 1 1350  
run 1600
```


- Clock with a period of 200 ns. CLK = 0 at 0ns, 1 at time 100 ns and repeats every 200 ns.
- Forcing x inputs. X = 0010 1001.

HDL models of sequential circuits

```
force CLK 0 0, 1 100 -repeat 200
```

```
force X 0 0, 1 350, 0 550, 1 750, 0 950, 1 1350
```

```
run 1600
```

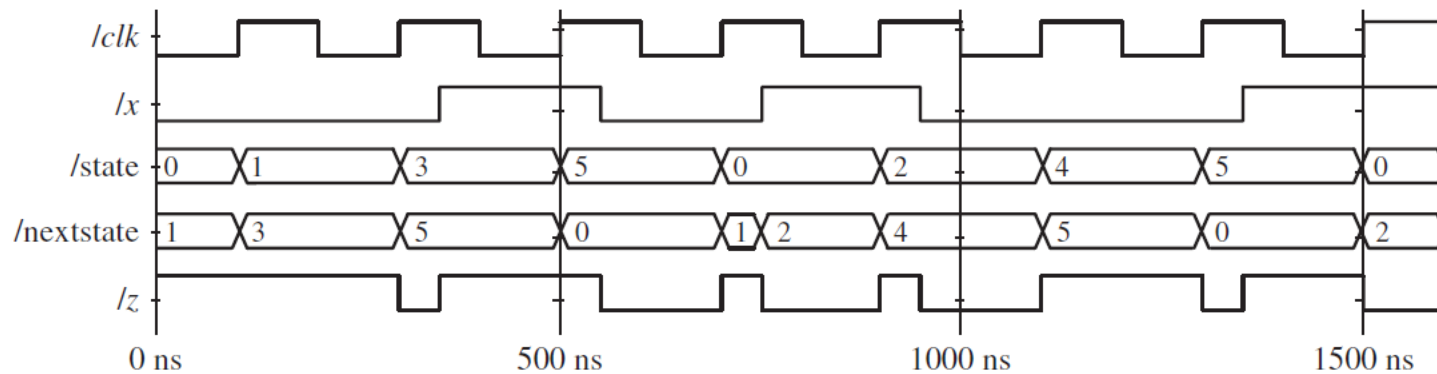

HDL models of sequential circuits

- Several ways to model sequential machines.
- One approach two always blocks – represent the two parts of the circuit.
- One always block models the combinational part of the circuit – generates next state information and outputs.
- Other always block – models the state registers – update the state at the appropriate edge of the clock.
- Circuit output and next state can change – with state or input changes – sensitivity list includes both.

HDL models of sequential circuits


```
always @ (posedge CLK)           // State Register
begin                             // (synthesis)
    State <= Nextstate;          // rising edge of clock
end
```

- Manual design of the state machine – behavioral description – may not result in exactly same circuit.
- State assignment.


HDL models of sequential circuits

- Another approach to create Verilog module – structural description of flip-flops and gates.
- Designer manually performs the design – obtain gate level circuitry in order to create a model.
- Specification of components and interconnections by designers – synthesizer tool does not have to translate any structural description.
- More control over the generated circuitry with structural description – lot more effort to produce a structural model.

HDL models of sequential circuits

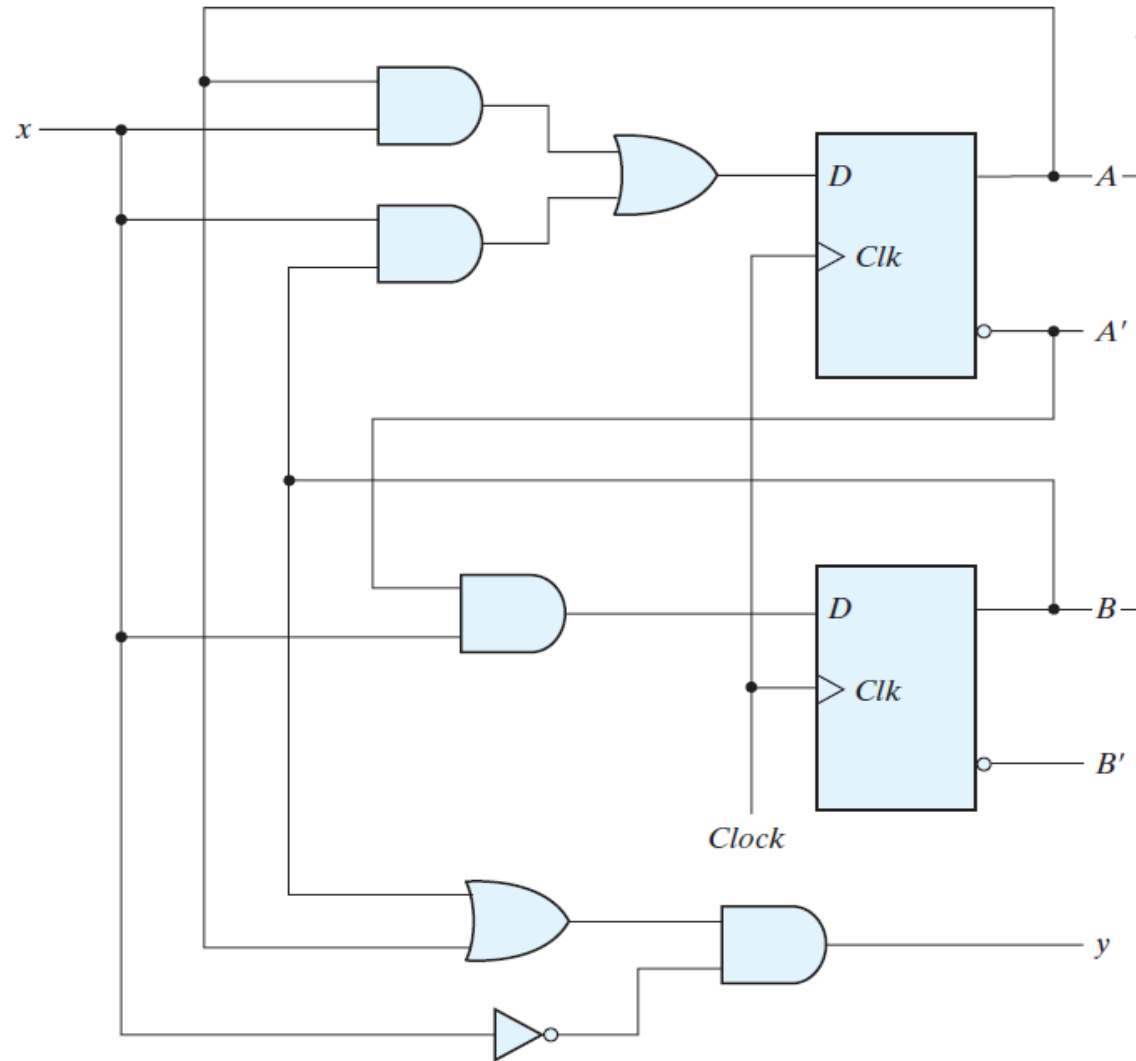

HDL models of sequential circuits

 

HDL models of sequential circuits

// Mealy FSM zero detector

```
module Mealy_Zero_Detector (output reg y_out, input  
x_in, clock, reset);  
  
reg [1: 0] state, next_state;  
parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;  
  
always @ ( posedge clock, negedge reset)  
  
if (reset == 0) state <= S0;  
else state <= next_state;
```

HDL models of sequential circuits

```
always @ (state, x_in)           // Form the next state
case (state)
S0:   if (x_in) next_state = S1; else next_state = S0;
S1:   if (x_in) next_state = S3; else next_state = S0;
S2:   if (~x_in) next_state = S0; else next_state = S2;
S3:   if (x_in) next_state = S2; else next_state = S0;
endcase
```

```
always @ (state, x_in)           // Form the Mealy output
case (state)
S0:   y_out = 0;
S1, S2, S3: y_out = ~x_in;
endcase
endmodule
```


HDL models of sequential circuits

- First always statement – resets the circuit to the initial state $S0 = 00$ – specifies synchronous clocked operation.
- At every rising edge of the clock – reset not equal to 0, state of the machine updated by first always block.
- Change in state detected by the sensitivity list mechanism of second always block – updates the value of next state – will be used by the first always block in the next clock cycle.
- Third always block detects change in state – updates the value of the output.

HDL models of sequential circuits

- Second and third always block responds to changes in x input – update the next state and y-out accordingly.

initial

begin

t_clock = 0;

forever #5 t_clock = ~t_clock;

end

initial

fork

t_reset = 0;

#2 t_reset = 1;

#87 t_reset = 0;

#89 t_reset = 1;

#10 t_x_in = 1;

#30 t_x_in = 0;

#40 t_x_in = 1;

#50 t_x_in = 0;

#52 t_x_in = 1;

#54 t_x_in = 0;

#70 t_x_in = 1;

#80 t_x_in = 1;

#70 t_x_in = 0;

#90 t_x_in = 1;

#100 t_x_in = 0;

#120 t_x_in = 1;

#160 t_x_in = 0;

#170 t_x_in = 1;


join

endmodule

© 2012 by NITK

HDL models of sequential circuits

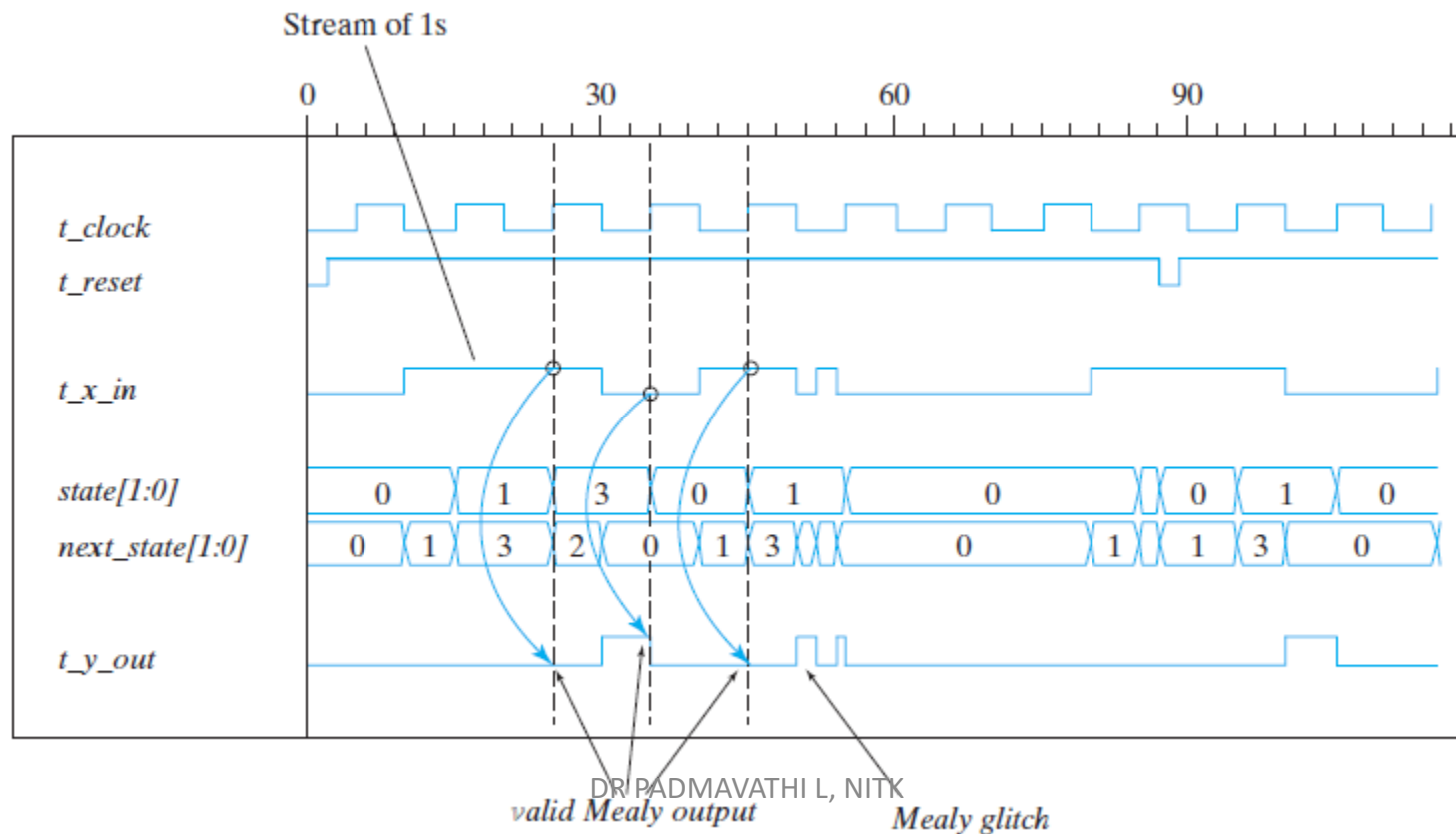- Notice how output responds to changes in both the state and the input.
- Look for transient logic and glitches



HDL models of sequential circuits

- fork...join construct
- Statements within the fork...join block execute in parallel.
- Time delays are relative to a common reference of $t = 0$ – time at which the block begins execution.
- Reset can be triggered on the fly – machine recovers from an unexpected reset condition during any state.


HDL models of sequential circuits

- First always block – corresponds to D flip-flop implementation of state registers.
- Second always block – combinational logic block describing the next state.
- Third always block – output combinational logic of the Mealy machine.
- Register operation of the state transition – uses non-blocking assignment operator `<=` – FFs of a sequential machine updated concurrently by a common clock.


HDL models of sequential circuits

- Second and third always block uses blocking assignment operator. (=)
- Sensitivity list – includes both the state and the input – logic must respond to change in either or both of them.
- Commonly used Verilog model of Mealy machine – close relationship to the state diagram of the machine.
- Simpler and more readable description.

HDL models of sequential circuits

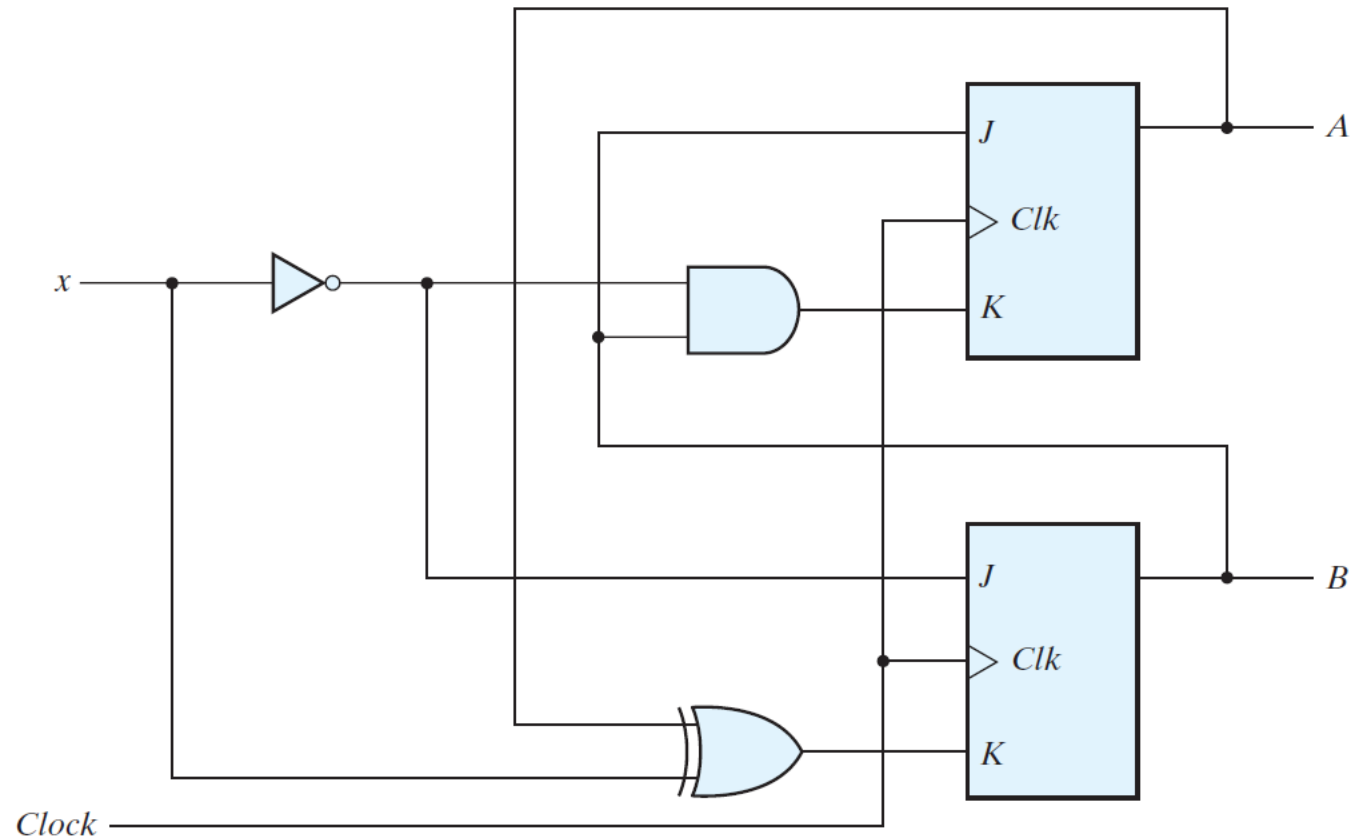

HDL models of sequential circuits

 

HDL models of sequential circuits

// Moore model FSM

```
module Moore_Model (output [1: 0] y_out, input x_in,  
clock, reset);
```

```
reg [1: 0] state;
```

```
parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
```

```
always @ ( posedge clock, negedge reset)
```

```
if (reset == 0) state <= S0; // Initialize to state S0
```

```
else case (state)
```

```
S0: if (~x_in) state <= S1; else state <= S0;
```

HDL models of sequential circuits

```
S1: if (x_in) state <= S2; else state <= S3;  
S2: if (~x_in) state <= S3; else state <= S2;  
S3: if (~x_in) state <= S0; else state <= S3;  
endcase
```

```
assign y_out = state; // Output of fl ip-fl ops
```

```
endmodule
```

HDL models of sequential circuits

Alternate style – state transitions of the machine described by a single clocked cyclic behavior – one always block.


Present state – identified by the variable state.

State transitions triggered by the rising edge of the clock – according to the conditions listed in the case statement.

Moor machine – output is independent of the input.

2 bit y output specified as a continuous assignment.


HDL models of sequential circuits

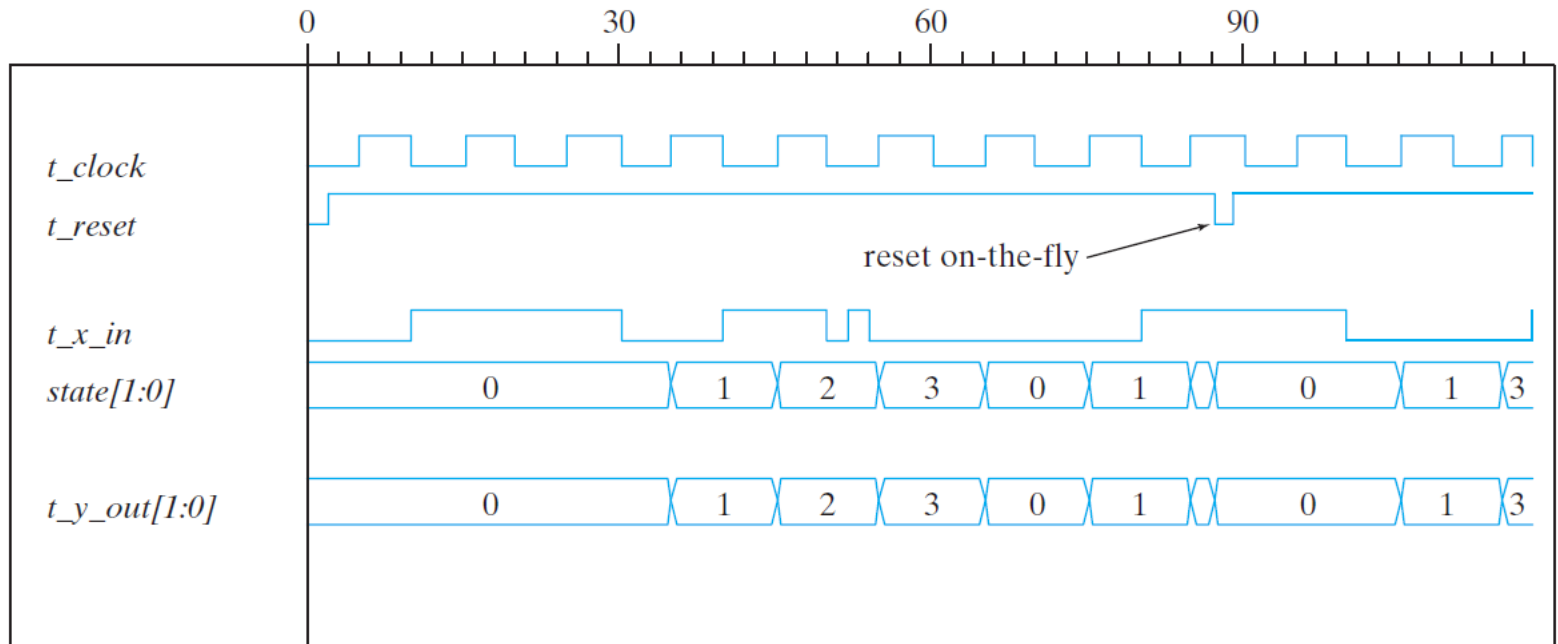


Output depends only on the present state of the input.

Reset on the fly – forces the state of the machine back to S0(00).

HDL models of sequential circuits

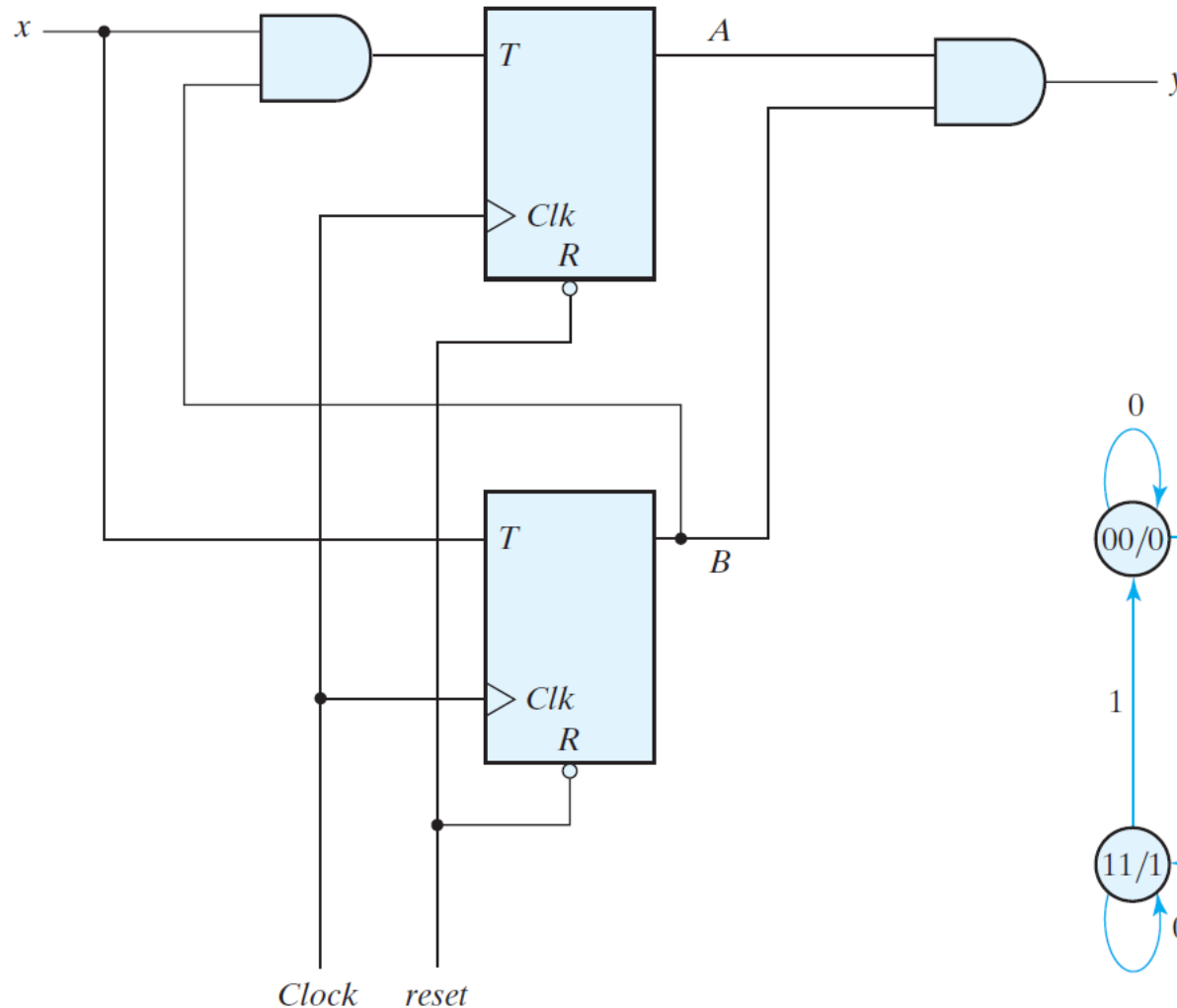

(a) Circuit diagram

 

(b) State diagram

HDL models of sequential circuits

// State-diagram-based model

```
module Moore_Model(output y_out, input x_in, clock,
reset);

reg [1: 0] state;

parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;

always @ ( posedge clock, negedge reset)
if (reset == 0) state <= S0;           // Initialize to state S0

else case (state)
S0: if (x_in) state <= S1; else state <= S0;
```

HDL models of sequential circuits

```
S1: if (x_in) state <= S2; else state <= S1;
```

```
S2: if (x_in) state <= S3; else state <= S2;
```

```
S3: if (x_in) state <= S0; else state <= S3;
```

```
endcase
```

```
assign y_out = state ;      // Output of fl ip-fl ops
```

```
endmodule
```

HDL models of sequential circuits

// Structural model

```
module Moore_Model_STR (output y_out, A, B, input x_in,  
clock, reset);
```

```
wire TA, TB;
```

// Flip-fl op input equations

```
assign TA = x_in & B;
```

```
assign TB = x_in;
```


HDL models of sequential circuits

// Output equation

assign y_out = A & B;

// Instantiate Toggle flip-flops

Toggle_flip_flop_3 M_A (A, TA, clock, reset);

Toggle_flip_flop_3 M_B (B, TB, clock, reset);

endmodule

HDL models of sequential circuits

```
module Toggle_flip_flop (Q, T, CLK, RST_b);
```

```
output Q;
```

```
input T, CLK, RST_b;
```

```
reg Q;
```

```
always @ ( posedge CLK, negedge RST_b)
```

```
if (RST_b == 0) Q <= 1'b0;
```

```
else if (T) Q <= ~Q;
```

```
endmodule
```

HDL models of sequential circuits

- Continuous assignment statement and corresponding Boolean expressions.
- Instantiated T FFs use TA and TB – defined by the input equations.

HDL models of sequential circuits

```
initial #200 $finish ;
```

```
initial begin
```

```
t_reset = 0;
```

```
t_clock = 0;
```

```
#5 t_reset = 1;
```

```
repeat (16)
```

```
#5 t_clock = ~t_clock;
```

```
end
```

```
initial begin
```

```
t_x_in = 0;
```

```
#15 t_x_in = 1;
```

```
repeat (8)
```

```
#10 t_x_in = ~t_x_in;
```

```
end
```

HDL models of sequential circuits

